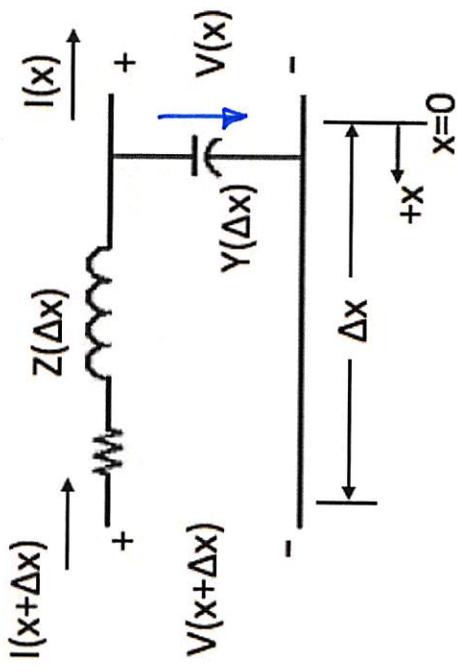


Defining the Differential Eq.

Consider a differential length of line:

$$\begin{aligned}V_{(X+\Delta X)} &= V_{(X)} + Z_{\Delta X} \cdot I_{(X+\Delta X)} \\I_{(X+\Delta X)} &= I_X + Y_{\Delta X} \cdot V_X\end{aligned}$$



$$\begin{aligned}\frac{I_{(X+\Delta X)} - I_X}{\Delta X} &= Z_{\Delta X} \cdot I_{(X+\Delta X)} \\ \lim_{\Delta X \rightarrow 0} \frac{dV}{dX} &= Z \cdot I_X \\ \frac{I_{(X+\Delta X)} - I_X}{\Delta X} &= Y_{\Delta X} \cdot V_X \\ \lim_{\Delta X \rightarrow 0} \frac{dI}{dX} &= Y \cdot V_X\end{aligned}$$

Solving the Diff Eq


$$\left[\frac{e^{+\gamma l} + e^{-\gamma l}}{2} \right] = \cosh(\gamma l) \quad \left[\frac{e^{+\gamma l} - e^{-\gamma l}}{2} \right] = \sinh(\gamma l)$$

$$V_S = \cosh(\gamma l) \cdot V_R + Z_C \sinh(\gamma l) \cdot I_R$$

$$I_S = \frac{1}{Z_C} \sinh(\gamma l) \cdot V_R + \cosh(\gamma l) \cdot I_R$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cosh(\gamma l) & Z_C \cdot \sinh(\gamma l) \\ \frac{1}{Z_C} \sinh(\gamma l) & \cosh(\gamma l) \end{bmatrix}$$

Example

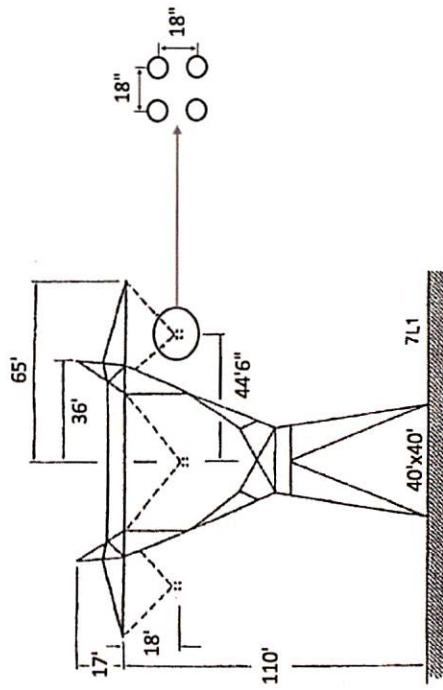

A 765 kV transmission line is 400km long.
The "flat" configuration features 4 Canary
conductors spaced at the corners of a square
18" per side. The bundles spacing is 44'6".

Per Table A4:

$$\text{Outside Diameter} = 1.162"$$

$$\text{GMR} = 0.0391'$$

$$R_{50C\ 60Hz} = 0.1185 \text{ ohms/mile}$$

Example

Per Table A4:

$$\text{Outside Diameter} = 1.162''$$

$$GMR = 0.0391'$$

$$R50C 60\text{Hz} = 0.1185 \text{ ohms/mile}$$

$$D_{eq} = \sqrt[3]{44.5 \cdot 44.5 \cdot 89} = 56.066 \text{ feet}$$

R'_{b_L}

$$D_{SL} = \sqrt[4]{1.5 \cdot 1.5 \cdot 1.5 \sqrt{2} \cdot 0.0391} = 0.65727 \text{ feet}$$


$$D_{SC} = \sqrt[4]{1.5 \cdot 1.5 \cdot 1.5 \sqrt{2} \cdot 1.162 / 24} = 0.69334 \text{ feet}$$

$$R = 0.1184 / 4 \Omega/\text{mile} \cdot 1\text{mile} / 1.609\text{km} = 0.0184 \Omega/\text{km}$$

$$X_L = j(2\pi \cdot 60) \cdot 2 \cdot 10^{-7} \ln \frac{56.066}{0.65727} = 3.35236 \cdot 10^{-4} \Omega/m \cdot 1000m/km = 0.335236 \Omega/km$$

$$Y = \frac{j(2\pi \cdot 60) \cdot (2\pi) 8.854 \cdot 10^{-12}}{\ln \frac{56.066}{0.69339}} = 4.77432 \cdot 10^{-9} \Omega/m \cdot 1000m/km = 4.77432 \cdot 10^{-6} \angle 90^\circ \Omega/km$$
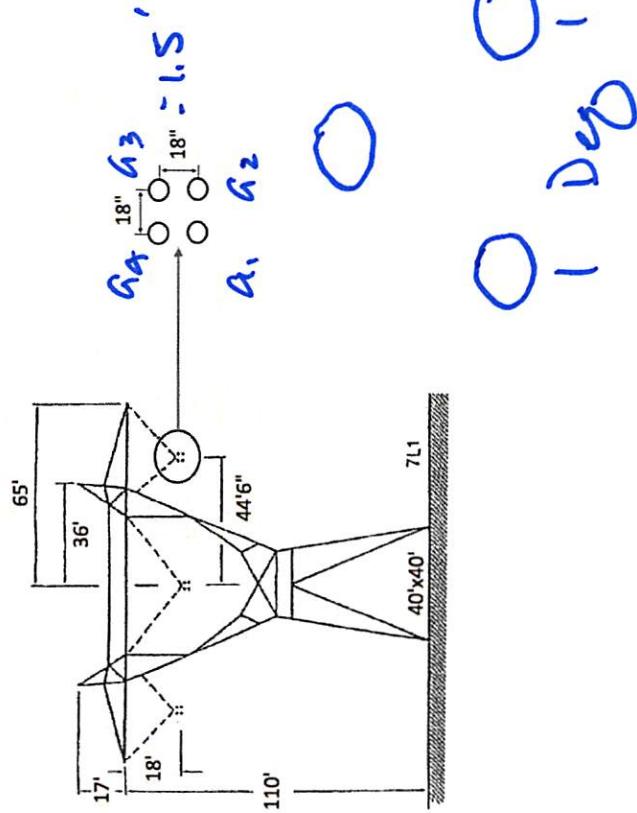
$$Z = 0.018395 + j0.335236 \Omega/km = 0.33574 \angle 86.859^\circ$$



Example

$$\gamma = \sqrt{ZY} = \sqrt{(0.33574 \angle 86.856^\circ)(4.77441 \cdot 10^{-6} \angle 90^\circ)} = 0.0012661 \angle 88.429^\circ / \text{km}$$

$$\gamma = 0.50643 \angle 88.4289^\circ$$

$$Z_C = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{(0.33574 \angle 86.856^\circ)}{(4.77441 \cdot 10^{-6} \angle 90^\circ)}} = 265.183 \angle -1.571^\circ$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cosh(\gamma l) & Z_C \cdot \sinh(\gamma l) \\ \frac{1}{Z_C} \sinh(\gamma l) & \cosh(\gamma l) \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 0.8747 \angle 0.4409^\circ & 128.6374 \angle 86.996^\circ \\ 1.8293 \cdot 10^{-3} \angle 90.137^\circ & 0.8747 \angle 0.4409^\circ \end{bmatrix}$$

Example

Given we're delivering 1000MVA at rated voltage, pf = 0.8 lagging

Determine the sending end voltage and current.

$$V_R \text{ (per phase)} = \frac{765000}{\sqrt{3}} = 441673\angle 0^\circ$$

$$I_R = \left(\frac{1000 \cdot 10^6 \angle 36.87^\circ}{\sqrt{3} \cdot 765000 \angle 0^\circ} \right)^* = 754.7 \angle -36.87^\circ$$

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} 0.8747 \angle 0.4409^\circ & 128.6374 \angle 86.996^\circ \\ 1.8293 \cdot 10^{-3} \angle 90.137^\circ & 0.8747 \angle 0.4409^\circ \end{bmatrix} \cdot \begin{bmatrix} 441673 \angle 0^\circ \\ 754.7 \angle -36.87^\circ \end{bmatrix} = \begin{bmatrix} 455202 \angle 9.8^\circ \\ 673.105 \angle 38.17^\circ \end{bmatrix}$$


$$S_{in} = 3 \cdot (455202 \angle 9.8^\circ)(673.105 \angle -38.17^\circ) = 919.196 \angle -28.37^\circ \text{ MVA}$$

$$S_{in} = 808.798 \text{MW} - j 436.768 \text{MVAR}$$

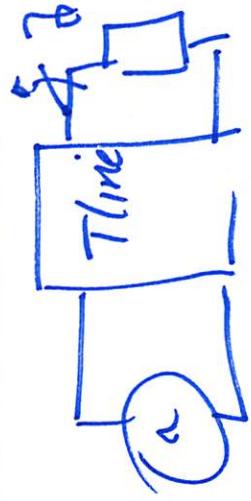Example

$$S_{out} = 1000 \angle 36.87^\circ MVA = 800MW + j600MVAR$$

$$\eta = \frac{P_{out}}{P_{in}} = \frac{800}{808.798} \cdot 100\% = 98.91\%$$



$|V_S| = 455202$ $|V_R| = 441763$ V_S is about 3% larger than V_R

however


$$V_S = AV_R + BI_R \quad \text{under no-load conditions } I_R = 0$$

$$|V_R \text{ no-load}| = \left| \frac{V_S}{A} \right| = \left| \frac{455202}{0.8747} \right| = 520409.28$$

$A = \cosh \gamma \lambda$

$$V_{REG} = \frac{V_{NL} - V_{FL}}{V_{FL}} \cdot 100\% = \frac{520409.28 - 441763}{441763} \cdot 100\% = 17.8\%$$

Lumped Parameter Network

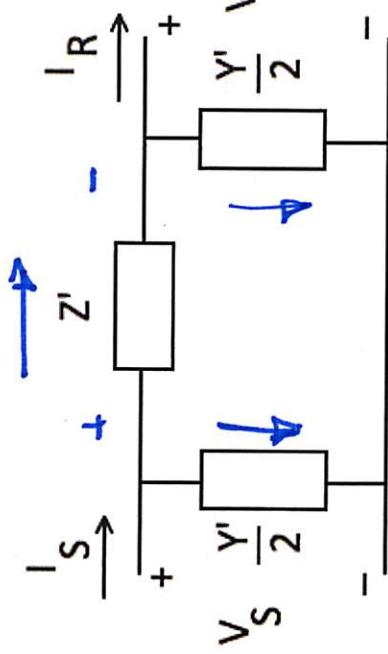

$$V_S = V_R + \left[V_R \left(\frac{Y'}{2} \right) + I_R \right] Z'$$

$$V_S = \left(1 + \frac{Z' Y'}{2} \right) V_R + Z' I_R$$



$$V_S = A V_R + B I_R$$

$$I_S = V_S \left(\frac{Y'}{2} \right) + V_R \left(\frac{Y'}{2} \right) + I_R$$

$$I_S = \left(\frac{Y'}{2} \right) \left(1 + \frac{Z' Y'}{2} \right) V_R + \left(\frac{Y'}{2} \right) Z' I_R + V_R \left(\frac{Y'}{2} \right) + I_R$$

$$I_S = \left(Y' + \frac{Z' Y'^2}{4} \right) V_R + \underbrace{\left(1 + \frac{Z' Y'}{2} \right) I_R}_{D I_R}$$

Lumped Parameter Network

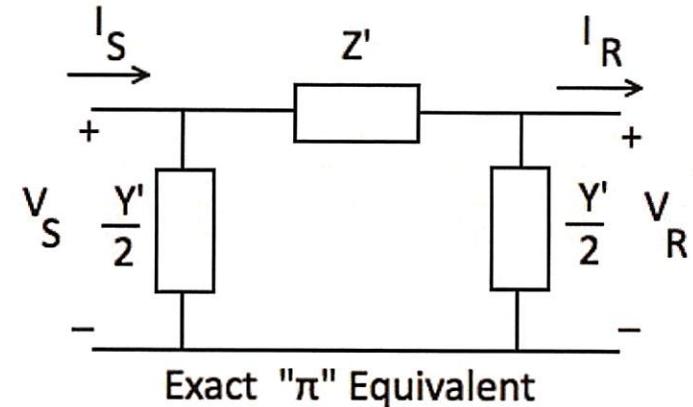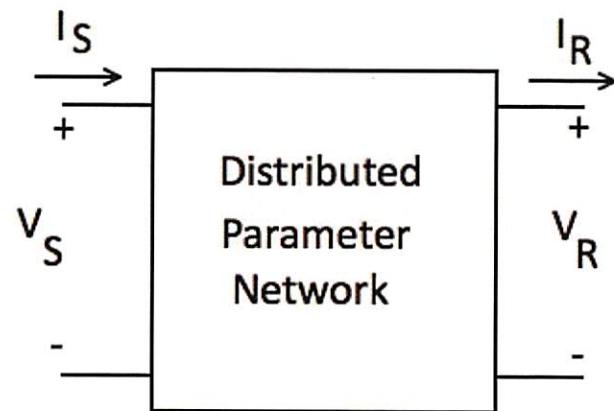

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cosh(\gamma l) & Z_C \cdot \sinh(\gamma l) \\ \frac{1}{Z_C} \sinh(\gamma l) & \cosh(\gamma l) \end{bmatrix}$$

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \left(1 + \frac{Z' Y'}{2}\right) & Z' \\ \left(Y' + \frac{Z' Y'^2}{4}\right) & \left(1 + \frac{Z' Y'}{2}\right) \end{bmatrix}$$

Lumped Parameter Network


$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cosh(\gamma l) & Z_C \cdot \sinh(\gamma l) \\ \frac{1}{Z_C} \sinh(\gamma l) & \cosh(\gamma l) \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \left(1 + \frac{Z'Y'}{2}\right) & Z' \\ Y' + \frac{Z'Y'^2}{4} & \left(1 + \frac{Z'Y'}{2}\right) \end{bmatrix}$$


$$Z' = Z_C \cdot \sinh(\gamma l)$$

$$\left(1 + \frac{Z'Y'}{2}\right) = \cosh(\gamma l) \quad \frac{Z'Y'}{2} = \cosh(\gamma l) - 1$$
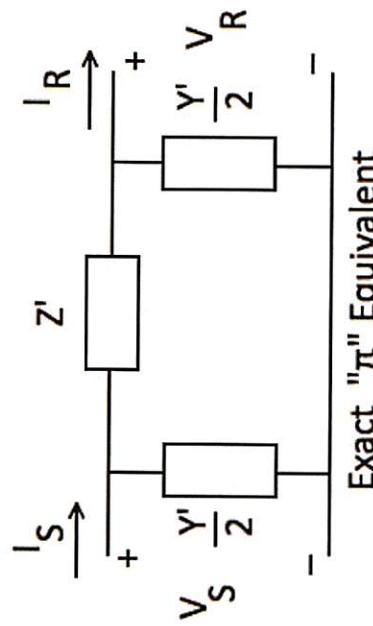
$$\frac{Y'}{2} = \frac{\cosh(\gamma l) - 1}{Z_C \cdot \sinh(\gamma l)} = \frac{1}{Z_C} \tanh\left(\frac{\gamma l}{2}\right)$$



Returning to our Example

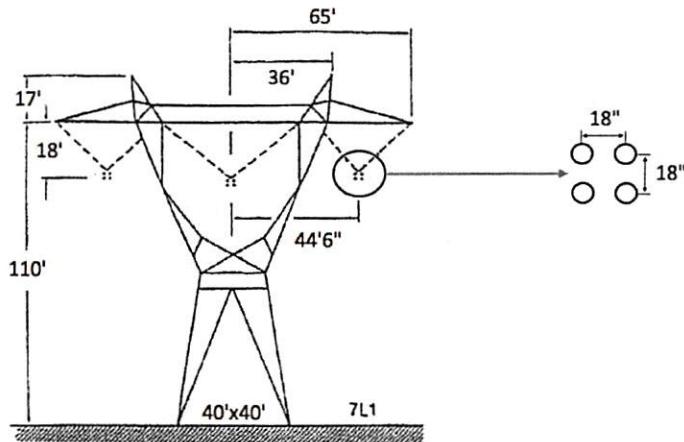

Per Table A4:
 Outside Diameter = 1.162" GMR = 0.0391'
 $R_{50C\ 60Hz} = 0.1185 \text{ ohms/mile}$

$$Y = 4.77432 \cdot 10^{-6} \angle 90^\circ \Omega/km$$

$$Z = 0.018412 + j0.335235 \Omega/km = 0.33574 \angle 86.859^\circ$$


$$\gamma = \sqrt{ZY} = \sqrt{(0.33574 \angle 86.859^\circ)(4.77432 \cdot 10^{-6} \angle 90^\circ)} = 0.0012661 \angle 88.430^\circ/km$$

$$\underline{\gamma l} = 0.50643 \angle 88.430^\circ \quad Z_C = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{(0.33574 \angle 86.859^\circ)}{(4.77432 \cdot 10^{-6} \angle 90^\circ)}} = 265.183 \angle -1.571^\circ$$

$$Z' = Z_C \sinh(\gamma l) = 265.183 \angle -1.571^\circ \sinh(0.50644 \angle 88.428^\circ) = 128.637 \angle 86.995^\circ \quad S$$

$$\frac{Y'}{2} = \frac{1}{Z_C} \tanh\left(\frac{\gamma l}{2}\right) = \frac{1}{265.183 \angle -1.571^\circ} \tanh\left(\frac{0.50644 \angle 88.428^\circ}{2}\right) = 9.758 \cdot 10^{-4} \angle 89.931^\circ \quad S$$

Lumped Parameter Solution

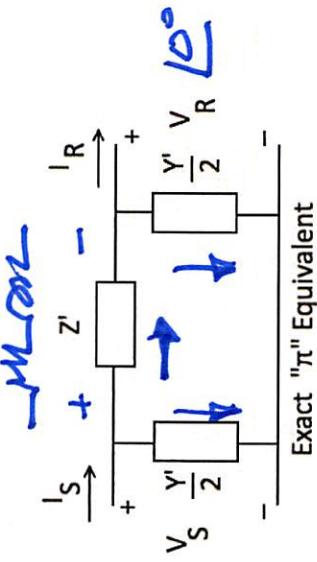

$$Z' = 128.6374 \angle 86.995^\circ \Omega$$

$$\frac{Y}{2} = 9.758 \cdot 10^{-4} \angle 89.931^\circ S$$

$$V_R (\text{per phase}) = \frac{765000}{\sqrt{3}} = 441673 \angle 0^\circ$$

$$I_R = \left(\frac{1000 \cdot 10^6 \angle 36.87^\circ}{\sqrt{3} \cdot 765000 \angle 0^\circ} \right)^* = 754.71 \angle -36.87^\circ A$$

$$I_{\frac{Y}{2}(R)} = 441673 \angle 0^\circ \cdot 9.758 \cdot 10^{-4} \angle 89.931^\circ S = 430.985 \angle 89.931^\circ A$$

$$I_{Z'} = I_R + I_{\frac{Y}{2}(R)} = 754.7 \angle -36.87^\circ + 430.985 \angle 89.931^\circ = 604.673 \angle -2.070 A$$

$$V_{Z'} = I_{Z'} \cdot Z' = 604.673 \angle -2.070 \cdot 128.6374 \angle 86.995^\circ \Omega = 77783.52 \angle 84.925^\circ V$$

$$V_S = V_{Z'} + V_R = 77783.52 \angle 84.925^\circ + 441673 \angle 0^\circ = 455195.38 \angle 9.80^\circ V$$

$$I_S = V_S \cdot \frac{Y}{2} + I_{Z'} = 455195.38 \angle 9.80^\circ \cdot 9.758 \cdot 10^{-4} \angle 89.931^\circ + 604.673 \angle -2.070 \\ = 673.102 \angle 38.167^\circ A$$

The Nominal Pi Equivalent Circuit

$$Z' = Z_C \sinh(\gamma l) = \sqrt{\frac{Z}{Y}} \sinh\left(\sqrt{ZY} \cdot l\right)$$

$$\sinh(x) = \left(x + \frac{x^3}{3!} + \frac{x^5}{5!} + \frac{x^7}{7!} + \dots \right)$$

$$Z' = \sqrt{\frac{Z}{Y}} \left[\left(\sqrt{ZY} \cdot l \right) + \frac{\left(\sqrt{ZY} \cdot l \right)^3}{3!} + \frac{\left(\sqrt{ZY} \cdot l \right)^5}{5!} + \dots \right]$$

$$Z' \approx \sqrt{\frac{Z}{Y}} \left(\sqrt{ZY} \cdot l \right) \approx \underline{Zl}$$

$$Z_{\text{nominal } \pi} = \underline{Zl}$$

The Nominal Pi Equivalent Circuit

$$\frac{Y'}{2} = \frac{\cosh(\gamma l) - 1}{Z_C \sinh(\gamma l)}$$

$$\cosh(x) = 1 + \frac{x^2}{2!} + \frac{x^4}{4!} + \frac{x^6}{6!} + \dots$$


$$\frac{Y'}{2} = \frac{\left[1 + \frac{(\sqrt{ZY} \cdot l)^2}{2!} + \cancel{\frac{(\sqrt{ZY} \cdot l)^4}{4!}} + \dots \right] - 1}{\sqrt{\frac{Z}{Y}} \left[(\sqrt{ZY} \cdot l) + \cancel{\frac{(\sqrt{ZY} \cdot l)^3}{3!}} + \cancel{\frac{(\sqrt{ZY} \cdot l)^5}{5!}} + \dots \right]}$$

$$\frac{Y'}{2} \approx \frac{\frac{(\sqrt{ZY} \cdot l)^2}{2}}{\sqrt{\frac{Z}{Y}} (\sqrt{ZY} \cdot l)} \approx \frac{\sqrt{ZY} \cdot l}{2 \cdot \sqrt{\frac{Z}{Y}}} \approx \frac{Y \cdot l}{2} = \frac{Y}{2}$$

S $\frac{Y}{2}_{\text{nominal } \pi} = \frac{Y \cdot l}{2}$

The Nominal Pi Equivalent Circuit
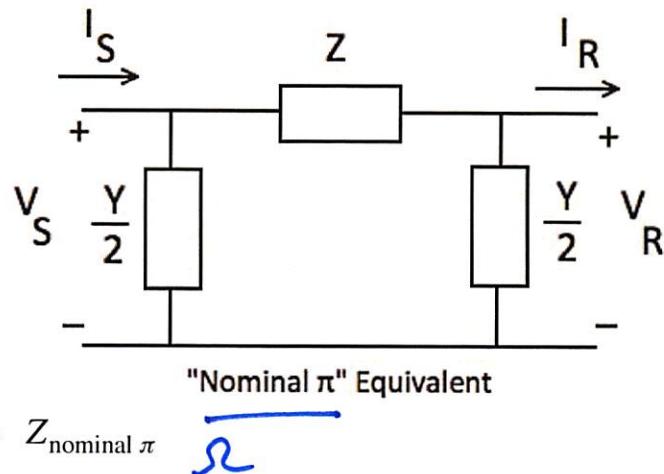
$$Z_{\text{nominal } \pi} = Zl \quad \frac{Y}{2 \text{ nominal } \pi} = \frac{Y \cdot l}{2}$$



$$Zl = 0.33574 \angle 86.995^\circ \cdot 400 = 134.296 \angle 86.995^\circ = Z_{\text{nominal } \pi}$$

S

$$\frac{Y \cdot l}{2} = \frac{4.77432 \cdot 10^{-6} \angle 90^\circ \cdot 400}{2} = 9.5486 \cdot 10^{-4} \angle 90^\circ = \frac{Y}{2 \text{ nominal } \pi} \quad \text{S}$$


Recall the exact parameters:

$$Z' = Z_C \sinh(\gamma l) = 265.183 \angle -1.571^\circ \sinh(0.50644 \angle 88.428^\circ) = 128.637 \angle 86.995^\circ \quad \text{S}$$

$$\frac{Y'}{2} = \frac{1}{Z_C} \tanh\left(\frac{\gamma l}{2}\right) = \frac{1}{265.183 \angle -1.571^\circ} \tanh\left(\frac{0.50644 \angle 88.428^\circ}{2}\right) = 9.758 \cdot 10^{-4} \angle 89.931^\circ$$

Short Line Approximation

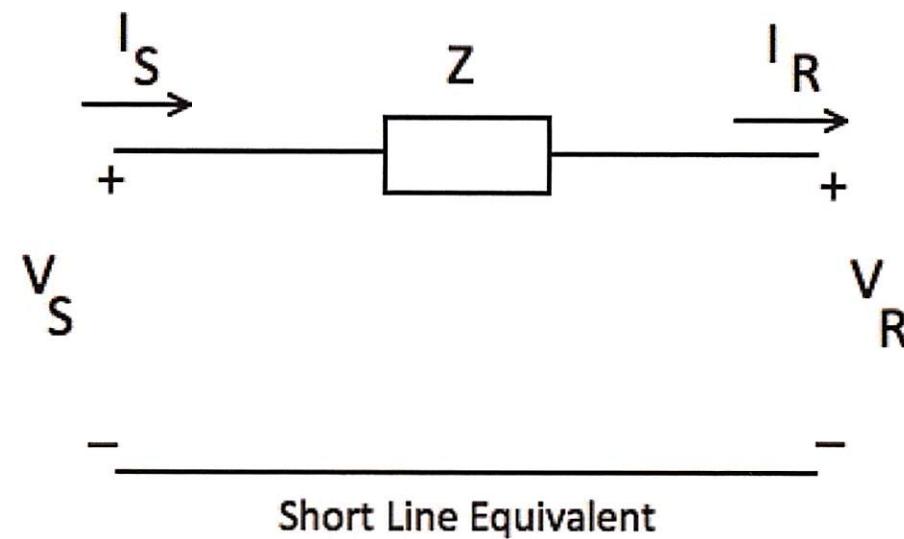Since the shunt admittance is normally quite small, as the line length gets small $Yl/2$ becomes negligible and $Y/2 \Rightarrow 0$. If the admittance approaches zero, the impedance approaches infinity. The short line equivalent circuit is shown below.



Three Lumped Parameter Line Models

Exact π

$$\begin{aligned}Z' &= Z_C \sinh(\gamma l) \\ \frac{Y'}{2} &= \frac{1}{Z_C} \tanh\left(\frac{\gamma l}{2}\right)\end{aligned}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}$$

$$\begin{bmatrix} \cosh(\gamma l) & Z_C \cdot \sinh(\gamma l) \\ \frac{1}{Z_C} \sinh(\gamma l) & \cosh(\gamma l) \end{bmatrix}$$

Nominal π

$$\begin{aligned}Z &= Zl \\ \frac{Y}{2} &= \frac{Yl}{2}\end{aligned}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}$$

$$\begin{bmatrix} \left(1 + \frac{ZY}{2}\right) & Z \\ \left(Y + \frac{ZY^2}{4}\right) & \left(1 + \frac{ZY}{2}\right) \end{bmatrix}$$

Short Line

$$\begin{aligned}Z &= Zl \\ \frac{Y}{2} &= 0\end{aligned}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}$$

$$\begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix}$$

How do I know what to use??



Line Length	Appropriate Model
80km or less	Short line
80km – 250km	Nominal π
greater than 250 km	Exact π

Or – whatever I tell you to use !!!

Table 5.1 pg 258
269

Michigan Tech

Comparison Calculations

400 km long line

	Exact	Nominal	Short
A=D	0.8747∠.4407	0.8720∠.4615	1.0000
Z' (Z)=B	128.6∠87.00	134.3∠86.86	134.3∠86.86
C	1.829x10 ⁻³ ∠90.14	1.665x10 ⁻³ ∠90.46	0.0000
Y'/2 (Y/2)	9.757x10 ⁻⁴ ∠89.93	9.548x10 ⁻⁴ ∠90.00	0.0000
V _s	455.2 kV ∠9.80	457.5 kV ∠10.2	512.8 kV ∠8.7
I _s	673.0∠38.16	627.0∠33.36	754.7∠-36.87

100 km long line

	Exact	Nominal	Short
A=D	0.9920∠.0253	0.9920∠.0254	1.0000
Z' (Z)=B	33.49∠86.87	33.58∠86.86	33.58∠86.86
C	4.761x10 ⁻⁴ ∠90.01	4.736x10 ⁻⁴ ∠90.03	0.0000
Y'/2 (Y/2)	2.390x10 ⁻⁴ ∠90.00	2.387x10 ⁻⁴ ∠90.00	0.0000
V _s	454.8 kV ∠2.464	454.9 kV ∠2.470	458.4 kV ∠2.427
I _s	644.9∠-21.72	645.2∠-21.81	754.7∠-36.87

	25 km long line		
	Exact	Nominal	Short
A=D	0.9995∠.00157	1.0000∠.0034	1.0000
Z' (Z)=B	8.392∠86.86	8.394∠86.86	8.394∠86.86
C	1.193x10 ⁻⁴ ∠90.00	1.194x10 ⁻⁴ ∠90.00	0.0000
Y'/2 (Y/2)	5.968x10 ⁻⁵ ∠90.00	5.968x10 ⁻⁵ ∠90.00	0.0000
V _s	445.6 kV ∠.625	445.7 kV ∠.627	445.8 kV ∠.624
I _s	723.9∠-33.5	724.3∠-33.5	754.7∠-36.87

765 kV line:

$$z = .33575∠86.86 \Omega/\text{km}$$

$$y = 4.7740 \times 10^{-6}∠90.00 \text{ S/km}$$

$$Z_C = 265.2∠-1.572 \Omega$$

$$\gamma = 1.266 \times 10^{-3}∠88.43 / \text{km}$$

$$V_R = 441,673 \text{ V/phase}$$

$$I_R = 754.7∠-36.87 \text{ A}$$

Lossless Lines

$$Z = 0.1\cancel{8}96 + j0.33524 \Omega/km$$

$$Y = j4.77432 \cdot 10^{-6} S/km$$

if we neglect R

$$Z = j0.33524 \Omega/km$$

$$Z_C = \sqrt{\frac{Z}{Y}} = 264.986 \Omega \quad \text{"Surge Impedance" of a lossless line (purely real)}$$

$$\gamma = \sqrt{ZY} = j0.0012649 / km = \alpha + j\beta \quad (\alpha = 0 \text{ purely imaginary})$$

$$\cosh(x) = \frac{e^x + e^{-x}}{2} \quad \cosh(j\beta) = \frac{e^{j\beta} + e^{-j\beta}}{2} = \cos(\beta)$$

$$\sinh(x) = \frac{e^x - e^{-x}}{2} \quad \sinh(j\beta) = \frac{e^{j\beta} - e^{-j\beta}}{2} = j \sin(\beta)$$

Lossless Lines

$$\begin{bmatrix} A_{(x)} & B_{(x)} \\ C_{(x)} & D_{(x)} \end{bmatrix} = \begin{bmatrix} \cos(0.0012649 \cdot x) & j264.986 \sin(0.0012649 \cdot x) \\ j\frac{1}{264.986} \sin(0.0012649 \cdot x) & \cos(0.0012649 \cdot x) \end{bmatrix}$$

but 1 radian = 57.296°

$$\begin{bmatrix} A_{(x)} & B_{(x)} \\ C_{(x)} & D_{(x)} \end{bmatrix} = \begin{bmatrix} \cos(0.072473 \cdot x^\circ) & j264.986 \sin(0.072473 \cdot x^\circ) \\ j\frac{1}{264.986} \sin(0.072473 \cdot x^\circ) & \cos(0.072473 \cdot x^\circ) \end{bmatrix}$$

converting to p.u. $V_{base} = 765kV$ and $S_{base} = 1000MVA$

$$Z_{base} = \frac{(765 \cdot 10^3)^2}{1000 \cdot 10^6} = 585.225$$

$$\begin{bmatrix} A_{(x)} & B_{(x)} \\ C_{(x)} & D_{(x)} \end{bmatrix} = \begin{bmatrix} \cos(0.072473 \cdot x^\circ) & j0.45279 \sin(0.072473 \cdot x^\circ) \\ j2.20851 \sin(0.072473 \cdot x^\circ) & \cos(0.072473 \cdot x^\circ) \end{bmatrix}$$


Lossless Line

$$V_{(x)} = A_{(x)} \cdot V_R + B_{(x)} \cdot I_R$$

$$V_{(x)} = \cos(0.072473 \cdot x^\circ) \cdot V_R + j264.986 \sin(0.072473 \cdot x^\circ) \cdot I_R$$

if we terminate the line with a surge impedance load

$$I_R = \frac{V_R}{Z_C}$$

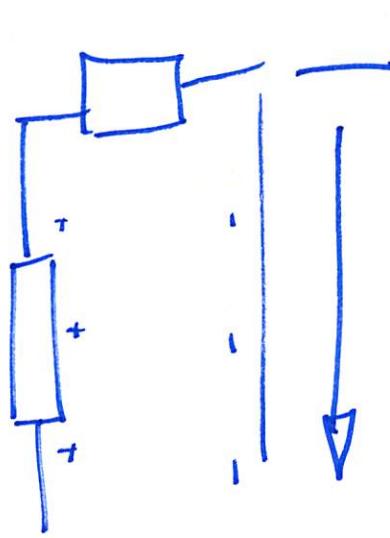

$$V_{(x)} = \cos(0.072473 \cdot x^\circ) \cdot V_R + j \sin(0.072473 \cdot x^\circ) \cdot V_R$$



$$V_{(x)} = [\cos(0.072473 \cdot x^\circ) + j \sin(0.072473 \cdot x^\circ)] \cdot V_R$$

$$V_{(x)} = (1 \angle 0.072473 \cdot x^\circ) \cdot V_R$$

$$\frac{765,000}{\sqrt{3}} \angle 10^\circ$$

$\chi = 0$

Lossless Line

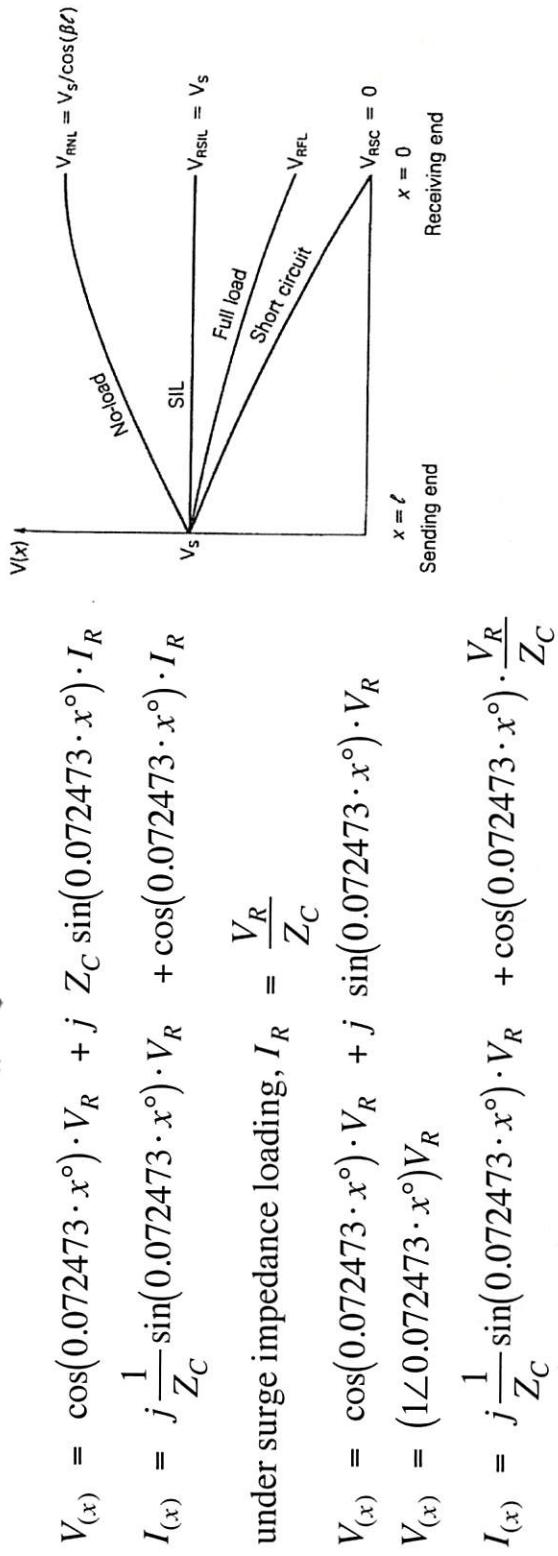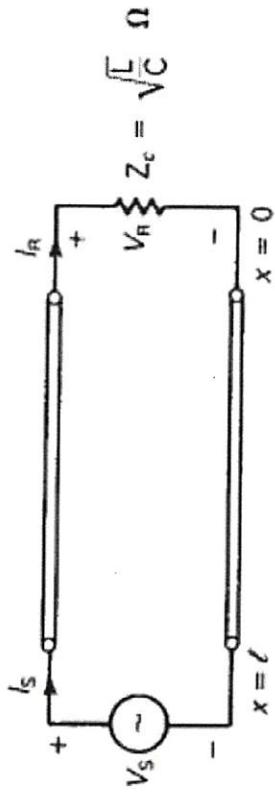

The real power flow is constant along the length of the line.
The reactive power flow is zero.

MichiganTech

Wavelength

$$V_{(x)} = (1 \angle 0.072473 \cdot x^\circ) \cdot V_R$$

$$V_{(x)} = (1 \angle 0.072473 \cdot (400)^\circ) \cdot V_R$$


$$V_{(x)} = (1 \angle 28.99^\circ) \cdot V_R$$

Wavelength is defined as the distance required to change the phase of the voltage or current by 360° .

$$0.072473 \cdot \lambda^\circ = 360^\circ \quad \lambda = 4,968 \text{ km} = 3088 \text{ miles}$$

Typical transmission lines are only a small fraction of a wavelength.

Steady State Stability Limit

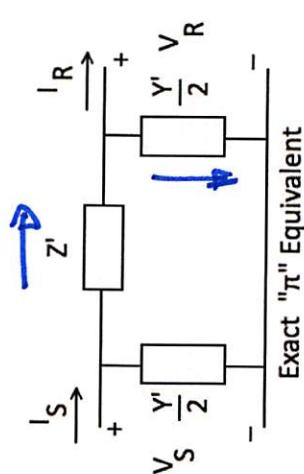

$$I_R = \frac{V_S - V_R}{Z} - \frac{Y}{2} \cdot V_R$$


$$S_R = V_R \cdot I_R^* = V_R \cdot \left(\frac{V_S - V_R}{Z} - \frac{Y}{2} \cdot V_R \right)^*$$

$$V_R = V_R \angle 0^\circ \quad V_S = V_S \angle \delta^\circ \quad Z = jX \quad \text{and} \quad Y = j\omega C l$$


$$S_R = V_R \left(\frac{V_S \angle \delta - V_R}{jX} \right)^* + \frac{j\omega C l}{2} V_R^2$$

$$S = P + jQ$$
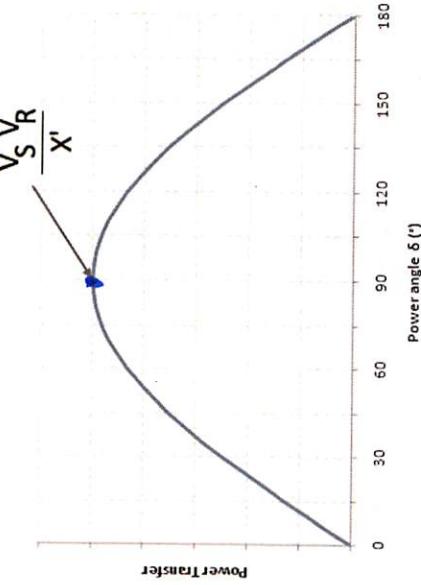
$$S_R = V_R \left(\frac{V_S \angle -\delta - V_R}{-jX} \right) + \frac{j\omega C l}{2} V_R^2$$




$$P_R = \frac{|V_R| \cdot |V_S|}{|X|} \cos(90 - \delta^\circ) = \frac{|V_R| \cdot |V_S|}{|X|} \sin \delta$$

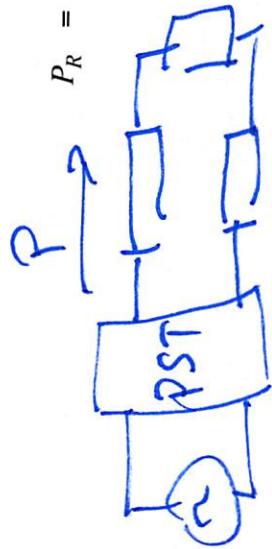

Michigan Tech


$\uparrow \downarrow \uparrow$

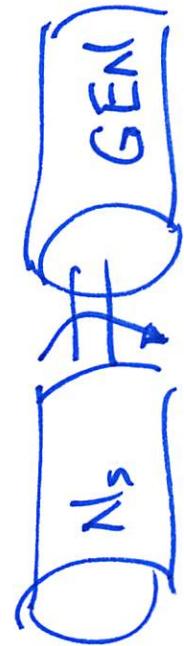Freq = $\tau \cdot N_s$ Steady State Stability Limit




$$f_0 = 60\text{Hz}$$

$$P_R = \frac{|V_R| \cdot |V_S|}{|X'|} \sin \delta$$

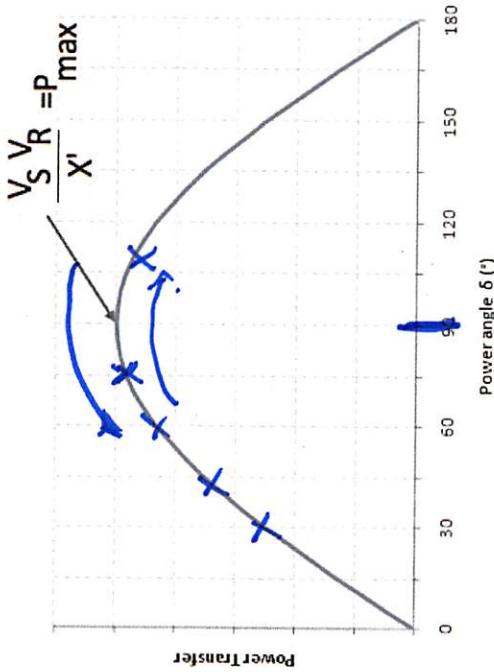


When $\delta = 90^\circ$, $\sin \delta = 1.0$ and $P_R = P_{R\ MAX}$
 $P_{R\ MAX}$ = the "theoretical steady state stability limit" of a lossless line.

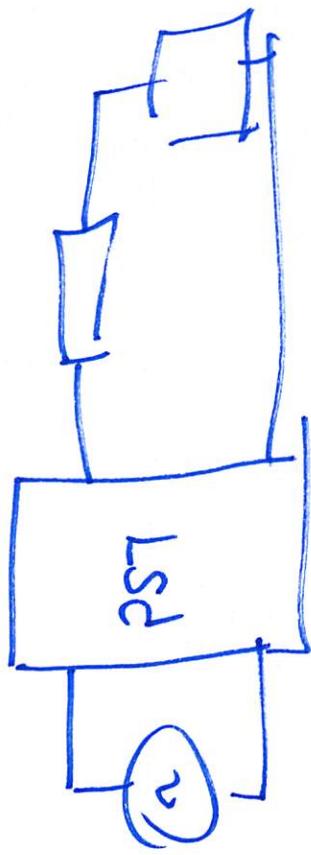If one were to try and exceed this limit the generators at the sending end of the line would lose synchronization with the machines on the receiving end of the line and that would be really really bad!




Exceeding The Stability Limit

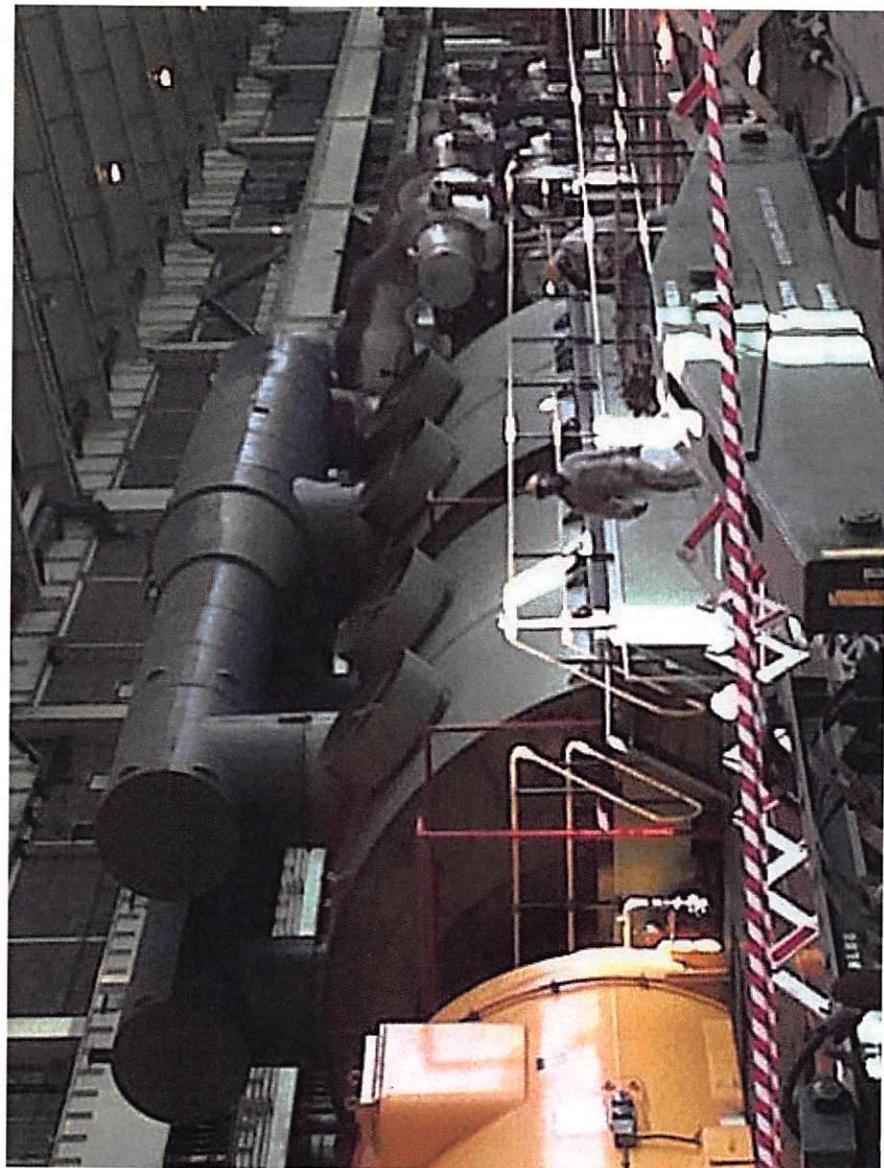


Michigan Tech

Exceeding the Stability Limit

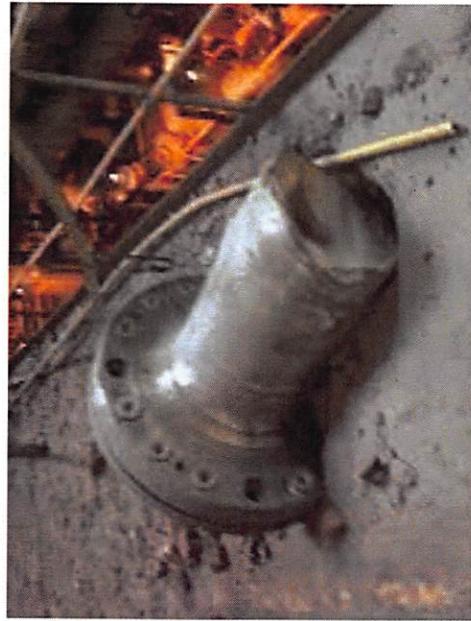

Michigan Tech

Exceeding the Stability Limit

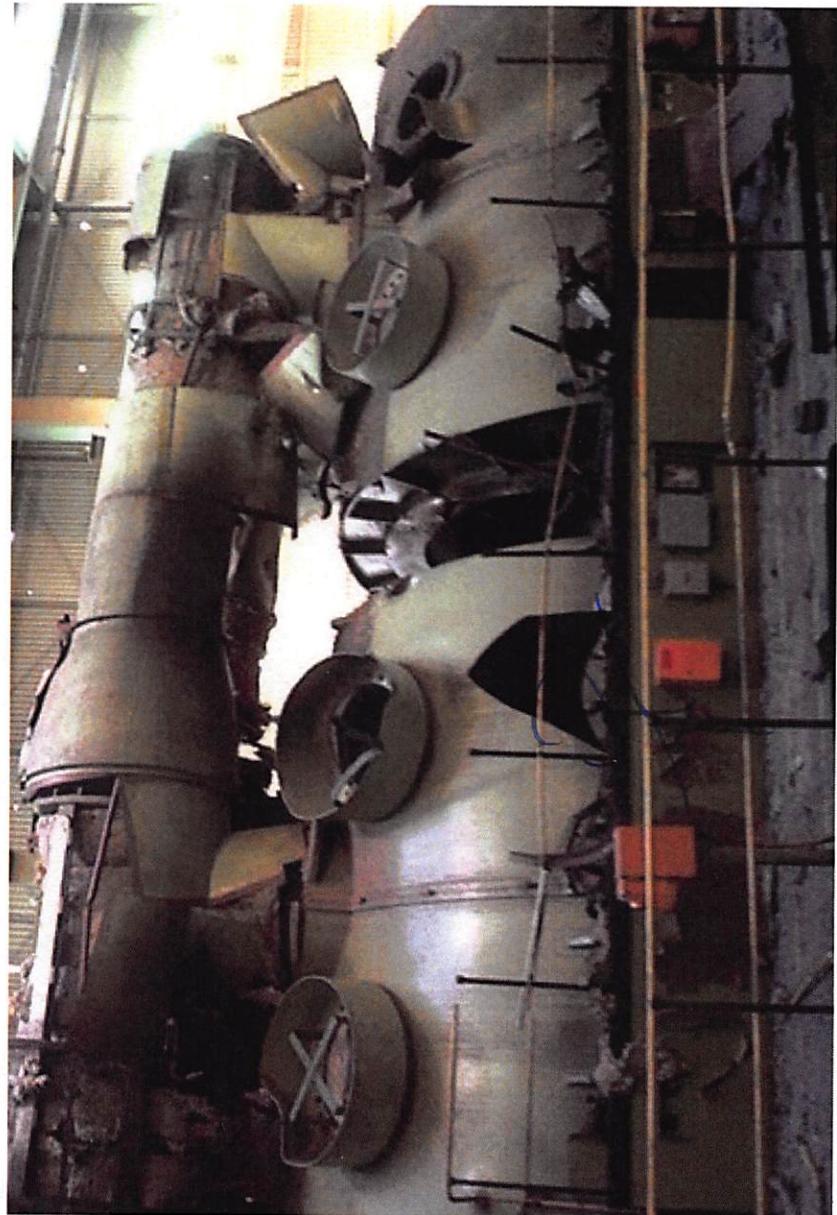

Michigan Tech