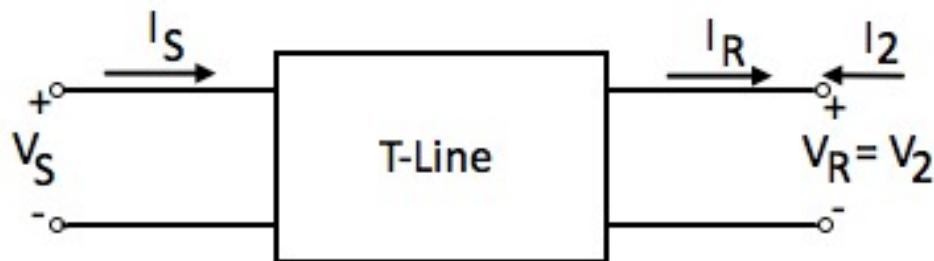


## Two Ports

---



$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

$$V_S = AV_R + BI_R$$

$$I_S = CV_R + DI_R$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Admittance parameters

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$


Z - parameters

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

h - parameters

## Two Ports

---

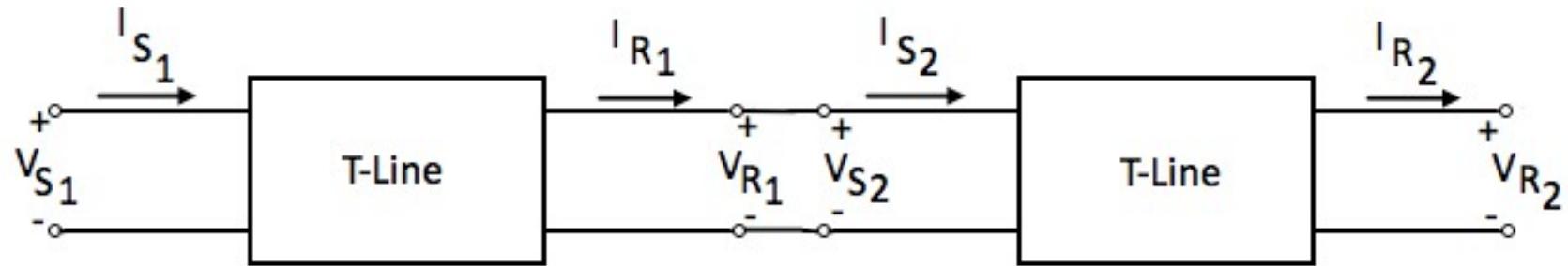


$$\begin{bmatrix} V_{S_1} \\ I_{S_1} \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} V_{R_1} \\ I_{R_1} \end{bmatrix} \quad \begin{bmatrix} V_{S_2} \\ I_{S_2} \end{bmatrix} = \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_{R_2} \\ I_{R_2} \end{bmatrix}$$

but  $\begin{bmatrix} V_{R_1} \\ I_{R_1} \end{bmatrix} = \begin{bmatrix} V_{S_2} \\ I_{S_2} \end{bmatrix}$

$$\begin{bmatrix} V_{S_1} \\ I_{S_1} \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_{R_2} \\ I_{R_2} \end{bmatrix}$$

# The Distributed Network



---

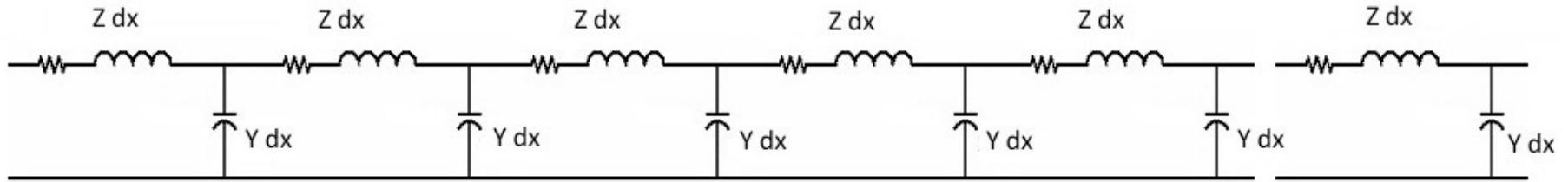

Let -  $Z_{\text{line (total)}} = 10\Omega$  and  $Y_{\text{line (total)}} = .1S$



Begin by dividing the line into  $n$  equal segments

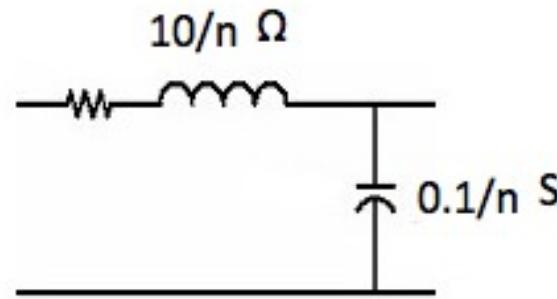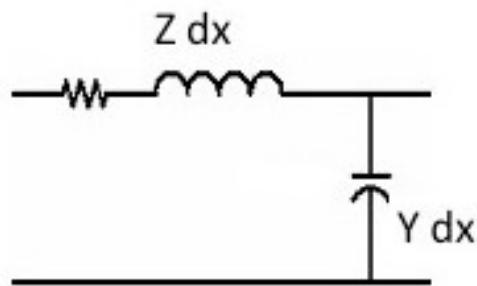The admittance and impedance per increment will be  $1/n$  th of the total



# The Distributed Network

---

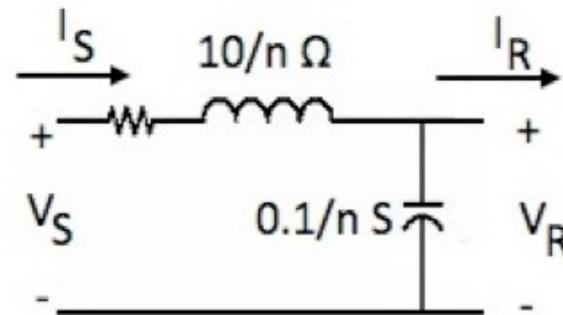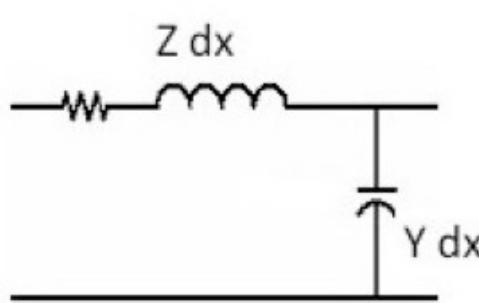

$$V_s = (10/n) I_s + V_R$$

$$I_s = I_R + V_R (0.1/n)$$

$$V_s = (10/n) (I_R + V_R (0.1/n)) + V_R = (1 + 1/n^2)V_R + (10/n)I_R$$


$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} \left(1 + \frac{1}{n^2}\right) & \frac{10}{n} \\ \frac{0.1}{n} & 1 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

# Distributed Network

---

For  $n = 1$

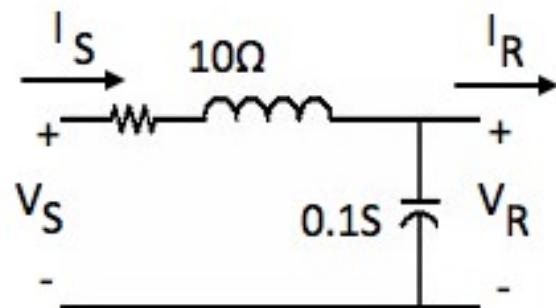
$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \left(1 + \frac{1}{n^2}\right) & \frac{10}{n} \\ \frac{0.1}{n} & 1 \end{bmatrix} = \begin{bmatrix} 2.0 & 10.0 \\ 0.1 & 1 \end{bmatrix}$$



$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} 2 & 10 \\ 0.1 & 1 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

# Distributed network

For  $n = 2$

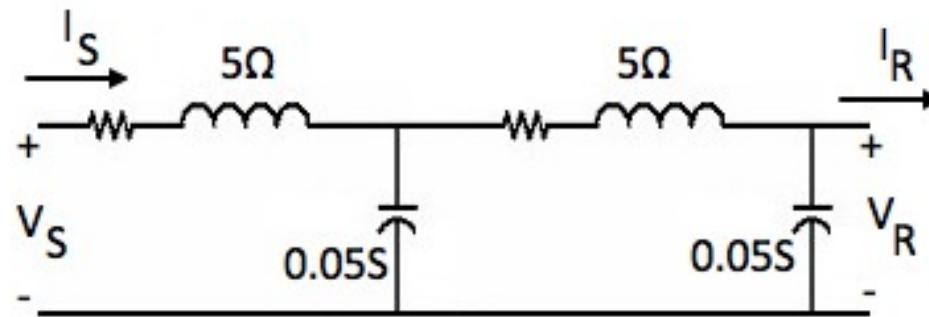


$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \left(1 + \frac{1}{n^2}\right) & \frac{10}{n} \\ \frac{0.1}{n} & 1 \end{bmatrix} = \begin{bmatrix} 1.25 & 5.0 \\ 0.05 & 1 \end{bmatrix}$$

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} 1.25 & 5.0 \\ 0.05 & 1 \end{bmatrix} \begin{bmatrix} 1.25 & 5.0 \\ 0.05 & 1 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix} = \begin{bmatrix} 1.8125 & 11.2500 \\ 0.1125 & 1.2500 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

# Distributed Network

For  $n = 4$

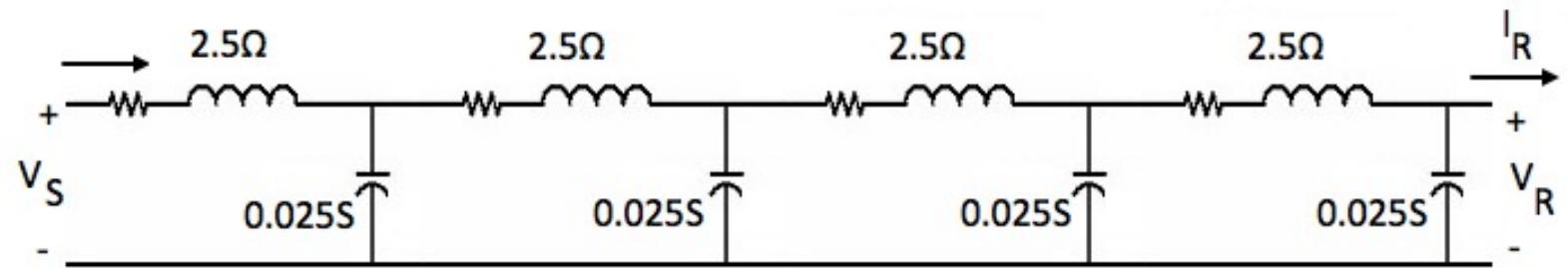

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \left(1 + \frac{1}{n^2}\right) & \frac{10}{n} \\ \frac{0.1}{n} & 1 \end{bmatrix} = \begin{bmatrix} 1.0625 & 2.5 \\ 0.025 & 1 \end{bmatrix}$$

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1.0625 & 2.5 \\ 0.025 & 1 \end{bmatrix} \begin{bmatrix} 1.0625 & 2.5 \\ 0.025 & 1 \end{bmatrix} \begin{bmatrix} 1.0625 & 2.5 \\ 0.025 & 1 \end{bmatrix} \begin{bmatrix} 1.0625 & 2.5 \\ 0.025 & 1 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix} = \begin{bmatrix} 1.6853 & 11.6217 \\ 0.1162 & 1.3948 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

# Distributed Network

---

For n = 8

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \left(1 + \frac{1}{n^2}\right) & \frac{10}{n} \\ \frac{0.1}{n} & 1 \end{bmatrix} = \begin{bmatrix} 1.0156 & 1.25 \\ 0.0125 & 1 \end{bmatrix}$$

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} 1.0156 & 1.25 \\ 0.0125 & 1 \end{bmatrix}^8 \begin{bmatrix} V_R \\ I_R \end{bmatrix} = \begin{bmatrix} 1.6156 & 11.7191 \\ 0.1172 & 1.4691 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

For n = 16

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \left(1 + \frac{1}{n^2}\right) & \frac{10}{n} \\ \frac{0.1}{n} & 1 \end{bmatrix} = \begin{bmatrix} 1.0039 & 0.625 \\ 0.00625 & 1 \end{bmatrix}$$

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} 1.0039 & 0.625 \\ 0.00625 & 1 \end{bmatrix}^{16} \begin{bmatrix} V_R \\ I_R \end{bmatrix} = \begin{bmatrix} 1.5796 & 11.7438 \\ 0.1174 & 1.5062 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

# Distributed Network

---

For n = infinity

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} 1.5431 & 11.7520 \\ 0.1175 & 1.5431 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

How do we know that???????




# Defining the Differential Eq.

Consider a differential length of line:

$$V_{(X+\Delta X)} = V_{(X)} + Z_{\Delta X} \cdot I_{(X+\Delta X)}$$
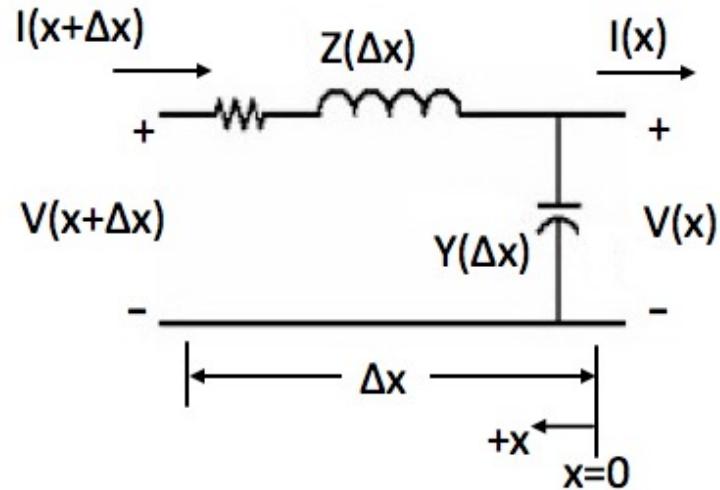
$$I_{(X+\Delta X)} = I_X + Y_{\Delta X} \cdot V_X$$



$$\frac{V_{(X+\Delta X)} - V_{(X)}}{\Delta X} = Z_{\Delta X} \cdot I_{(X+\Delta X)}$$

$$\lim_{\Delta X \rightarrow 0} \frac{dV}{dX} = Z \cdot I_X$$

$$\frac{I_{(X+\Delta X)} - I_X}{\Delta X} = Y_{\Delta X} \cdot V_X$$

$$\lim_{\Delta X \rightarrow 0} \frac{dI}{dX} = Y \cdot V_X$$

## Solving the Differential Eq.

---

$$\frac{dV}{dX} = Z_X \cdot I_X \quad \frac{dI}{dX} = Y \cdot V_X$$

$$s \cdot V_{(S)} - V(0^+) = Z \cdot I_{(S)}$$

$$s \cdot I_{(S)} - I(0^+) = Y \cdot V_{(S)}$$

$$s \cdot V_{(S)} - Z \cdot I_{(S)} = V(0^+)$$


$$s \cdot I_{(S)} - Y \cdot V_{(S)} = I(0^+)$$

$$\begin{bmatrix} s & -Z \\ -Y & s \end{bmatrix} \begin{bmatrix} V_{(S)} \\ I_{(S)} \end{bmatrix} = \begin{bmatrix} V(0^+) \\ I(0^+) \end{bmatrix}$$
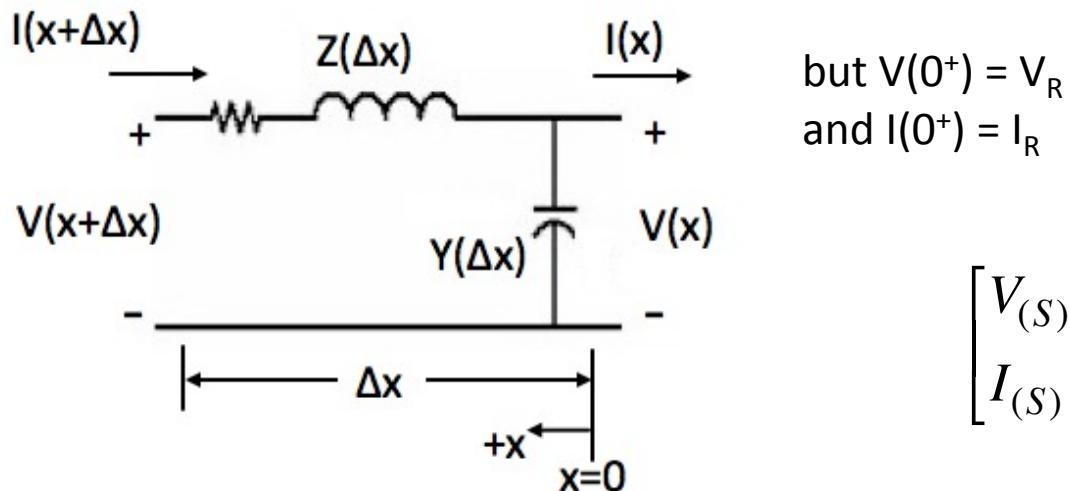
# Solving the Diff Eq.

$$\begin{bmatrix} s & -Z \\ -Y & s \end{bmatrix}^{-1} \begin{bmatrix} s & -Z \\ -Y & s \end{bmatrix} \begin{bmatrix} V_{(S)} \\ I_{(S)} \end{bmatrix} = \begin{bmatrix} s & -Z \\ -Y & s \end{bmatrix}^{-1} \begin{bmatrix} V(0^+) \\ I(0^+) \end{bmatrix}$$

$$\begin{bmatrix} V_{(S)} \\ I_{(S)} \end{bmatrix} = \left( \frac{1}{s^2 - YZ} \right) \begin{bmatrix} s & Z \\ Y & s \end{bmatrix} \begin{bmatrix} V(0^+) \\ I(0^+) \end{bmatrix}$$



$$\begin{bmatrix} V_{(S)} \\ I_{(S)} \end{bmatrix} = \left( \frac{1}{s^2 - YZ} \right) \begin{bmatrix} s & Z \\ Y & s \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

# Solving the Diff Eq

---

Expanding  $V_{(S)}$

$$V_{(S)} = \frac{sV_R + ZI_R}{s^2 - YZ} \text{ but } YZ = (\sqrt{YZ})^2 \text{ and } s^2 - (\sqrt{YZ})^2 = (s - \sqrt{YZ})(s + \sqrt{YZ})$$

$$V_{(S)} = \frac{sV_R + ZI_R}{(s - \sqrt{YZ})(s + \sqrt{YZ})} = \frac{A}{(s - \sqrt{YZ})} + \frac{B}{(s + \sqrt{YZ})}$$

$$sV_R + ZI_R = A(s + \sqrt{YZ}) + B(s - \sqrt{YZ}) = s(A + B) + (A - B)\sqrt{YZ}$$

$$V_R = A + B \quad \text{and} \quad \frac{ZI_R}{\sqrt{YZ}} = A - B \quad \text{or} \quad \sqrt{\frac{Z}{Y}}I_R = A - B$$

$$V_R + \sqrt{\frac{Z}{Y}}I_R = 2A \quad V_R - \sqrt{\frac{Z}{Y}}I_R = 2B$$

## Solving the Diff Eq

---

$$V_R + \sqrt{\frac{Z}{Y}} I_R = 2A \quad V_R - \sqrt{\frac{Z}{Y}} I_R = 2B$$

define characteristic impedance  $Z_C = \sqrt{\frac{Z}{Y}}$  and propagation constant  $\gamma = \sqrt{YZ} = \alpha + j\beta$

$$A = \frac{V_R}{2} + \frac{Z_C I_R}{2} \quad B = \frac{V_R}{2} - \frac{Z_C I_R}{2} \quad V_{(S)} = \frac{A}{(s - \sqrt{YZ})} + \frac{B}{(s + \sqrt{YZ})}$$

$$V_{(s)} = \frac{\frac{V_R}{2} + \frac{Z_C I_R}{2}}{s - \gamma} + \frac{\frac{V_R}{2} - \frac{Z_C I_R}{2}}{s + \gamma}$$

$$\text{LaPlace}^{-1} \left[ \frac{K}{s + a} \right] = K e^{-ax}$$

$$V_{(x)} = \left[ \frac{V_R}{2} + \frac{Z_C I_R}{2} \right] \cdot e^{+\gamma x} + \left[ \frac{V_R}{2} - \frac{Z_C I_R}{2} \right] \cdot e^{-\gamma x}$$

## Solving the Diff Eq

---

$$V_{(x)} = \left[ \frac{V_R}{2} + \frac{Z_C I_R}{2} \right] \cdot e^{+\gamma x} + \left[ \frac{V_R}{2} - \frac{Z_C I_R}{2} \right] \cdot e^{-\gamma x}$$

when  $x = l$  we are at the sending end of the line

$$V_s = \left[ \frac{V_R}{2} + \frac{Z_C I_R}{2} \right] \cdot e^{+\gamma l} + \left[ \frac{V_R}{2} - \frac{Z_C I_R}{2} \right] \cdot e^{-\gamma l}$$

$$V_s = \left[ \frac{e^{+\gamma l} + e^{-\gamma l}}{2} \right] V_R + \left[ \frac{e^{+\gamma l} - e^{-\gamma l}}{2} \right] Z_C I_R$$

Repeating the process and solving for  $I_S$  gives :

$$I_s = \left[ \frac{e^{+\gamma l} - e^{-\gamma l}}{2} \right] \frac{V_R}{Z_C} + \left[ \frac{e^{+\gamma l} + e^{-\gamma l}}{2} \right] I_R$$

# Solving the Diff Eq

---

$$V_s = \left[ \frac{e^{+\gamma l} + e^{-\gamma l}}{2} \right] V_R + \left[ \frac{e^{+\gamma l} - e^{-\gamma l}}{2} \right] Z_C I_R$$

$$I_s = \left[ \frac{e^{+\gamma l} - e^{-\gamma l}}{2} \right] \frac{V_R}{Z_C} + \left[ \frac{e^{+\gamma l} + e^{-\gamma l}}{2} \right] I_R$$

This looks somewhat familiar?    Eulers Identity??

$$\cos(x) = \frac{e^{+jx} + e^{-jx}}{2} \quad \sin(x) = \frac{e^{+jx} - e^{-jx}}{2j}$$

Not quite!

## Solving the Diff Eq

---

$$\left[ \frac{e^{+\gamma l} + e^{-\gamma l}}{2} \right] = \cosh(\gamma l) \quad \left[ \frac{e^{+\gamma l} - e^{-\gamma l}}{2} \right] = \sinh(\gamma l)$$


$$V_S = \cosh(\gamma l) \cdot V_R + Z_C \sinh(\gamma l) \cdot I_R$$

$$I_S = \frac{1}{Z_C} \sinh(\gamma l) \cdot V_R + \cosh(\gamma l) \cdot I_R$$


$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cosh(\gamma l) & Z_C \cdot \sinh(\gamma l) \\ \frac{1}{Z_C} \sinh(\gamma l) & \cosh(\gamma l) \end{bmatrix}$$

# The Hyperbolic Functions

---

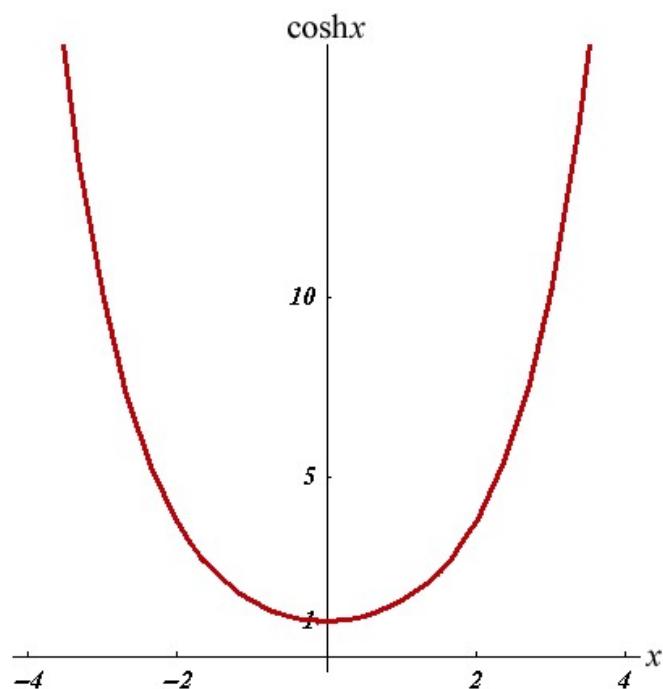

$$\cosh(x) = (e^x + e^{-x})/2$$

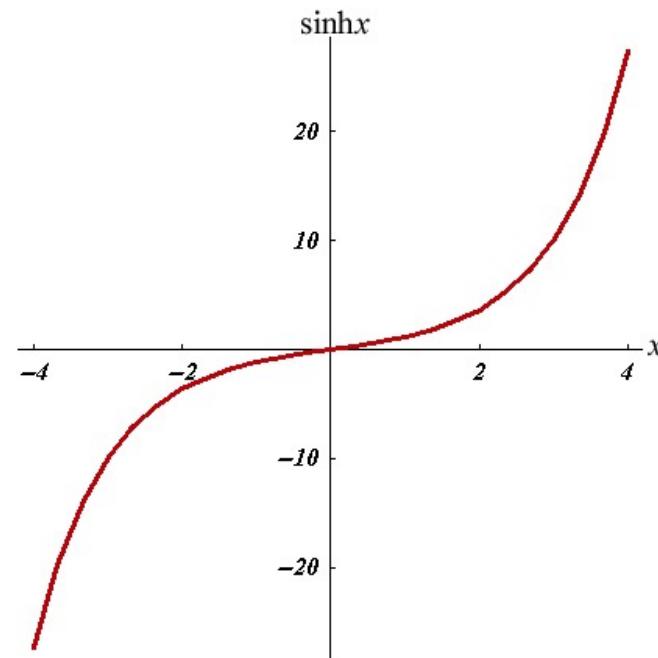

$$\sinh(x) = (e^x - e^{-x})/2$$

$$d/dx \cosh(x) = \sinh(x) \quad d/dx \sinh(x) = \cosh(x) \quad \text{and } \cosh^2(x) - \sinh^2(x) = 1$$

# Example

---

A transmission line is 100 football fields long:

The series impedance is  $0.1\Omega$  per football field (ohms per unit)  
The shunt admittance is  $.001S$  per football field (ohms $^{-1}$  per unit)

$$Z_C = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{0.1\Omega / \text{football field}}{0.001S / \text{football field}}} = 10\Omega$$

$$\gamma = \sqrt{ZY} = \sqrt{0.1 \cdot 0.001} = 0.01 / \text{football field}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cosh(\gamma l) & Z_C \cdot \sinh(\gamma l) \\ \frac{1}{Z_C} \sinh(\gamma l) & \cosh(\gamma l) \end{bmatrix}$$

$$A = D = \cosh((0.01)(100)) = 1.543081$$

$$B = 10 \sinh((0.01)(100)) = 11.752 \Omega$$

$$C = \frac{1}{10} \sinh((0.01)(100)) = .11752 S$$

# Warning – Warnung - 警告 – Varoitus - Onyo

---

You will need to be able to calculate  $\sinh(x)$ ,  $\cosh(x)$  and  $\tanh(x)$   
as well as  $\sinh^{-1}(x)$ ,  $\cosh^{-1}(x)$  and  $\tanh^{-1}(x)$

Where x is a complex number !!!!


$$\sinh(0.9\angle 80^\circ) = 0.7905\angle 82.79^\circ$$

$$\tanh(0.5\angle 75^\circ) = 0.5387\angle 72.35^\circ$$

$$\cosh^{-1}(0.8\angle 80^\circ) = 1.632\angle 63.56^\circ$$

# Example

---

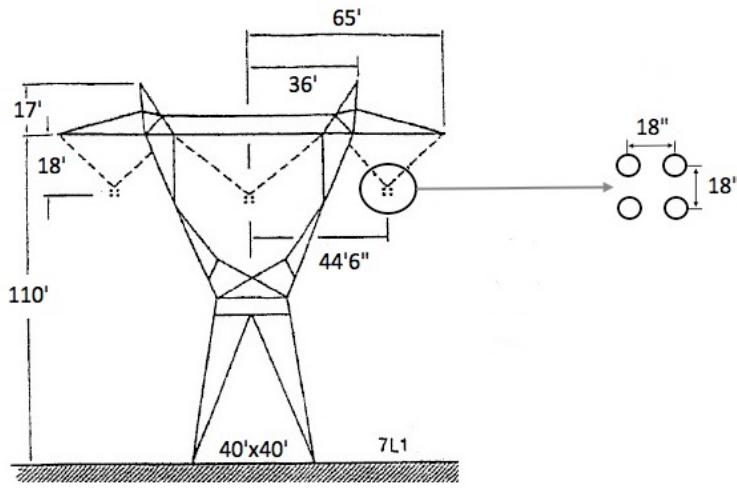

A 765 kV transmission line is 400km long. The “flat” configuration features 4 Canary conductors spaced at the corners of a square 18" per side. The bundles spacing is 44'6".

Per Table A4:

$$\text{Outside Diameter} = 1.162"$$

$$\text{GMR} = 0.0391'$$

$$R_{50C\ 60Hz} = 0.1185 \text{ ohms/mile}$$

# Example

---

Per Table A4:

Outside Diameter = 1.162"

GMR = 0.0391'

R50C 60Hz = 0.1185 ohms/mile

$$D_{eq} = \sqrt[3]{44.5 \cdot 44.5 \cdot 89} = 56.066 \text{ feet}$$

$$D_{SL} = \sqrt[4]{1.5 \cdot 1.5 \cdot 1.5 \sqrt{2} \cdot 0.0391} = 0.65727 \text{ feet}$$


$$D_{SC} = \sqrt[4]{1.5 \cdot 1.5 \cdot 1.5 \sqrt{2} \cdot 1.162 / 24} = 0.69334 \text{ feet}$$

$$R = 0.1184 / 4 \Omega/\text{mile} \cdot 1\text{mile}/1.609\text{km} = 0.0184 \Omega/\text{km}$$

$$X_L = j(2\pi \cdot 60) \cdot 2 \cdot 10^{-7} \ln \frac{56.066}{0.65727} = 3.35236 \cdot 10^{-4} \Omega/m \cdot 1000m/km = 0.335236 \Omega/km$$

$$Y = \frac{j(2\pi \cdot 60) \cdot (2\pi) 8.854 \cdot 10^{-12}}{\ln \frac{56.066}{0.69339}} = 4.77432 \cdot 10^{-9} \Omega/m \cdot 1000m/km = 4.77432 \cdot 10^{-6} \angle 90^\circ \Omega/km$$
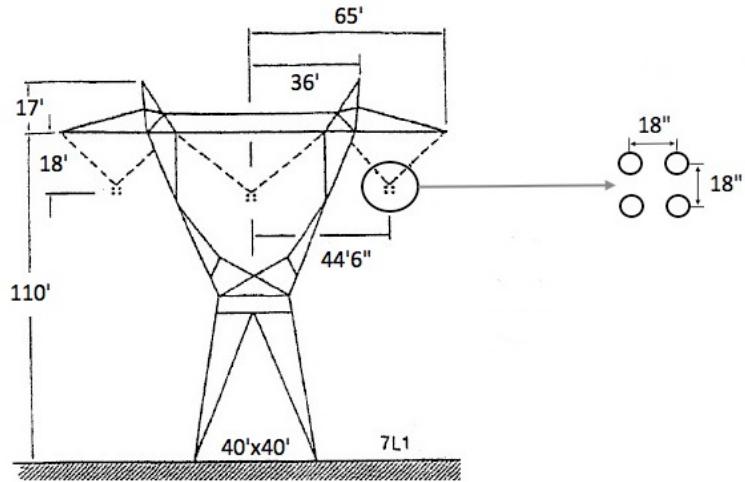
$$Z = 0.018395 + j0.335236 \Omega/km = 0.33574 \angle 86.859^\circ$$



## Example

---

$$\gamma = \sqrt{ZY} = \sqrt{(0.33574 \angle 86.856^\circ)(4.77441 \cdot 10^{-6} \angle 90^\circ)} = 0.0012661 \angle 88.429^\circ / km$$

$$\gamma l = 0.50643 \angle 88.4289^\circ$$

$$Z_C = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{(0.33574 \angle 86.856^\circ)}{(4.77441 \cdot 10^{-6} \angle 90^\circ)}} = 265.183 \angle -1.571^\circ$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cosh(\gamma l) & Z_C \cdot \sinh(\gamma l) \\ \frac{1}{Z_C} \sinh(\gamma l) & \cosh(\gamma l) \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 0.8747 \angle 0.4409^\circ & 128.6374 \angle 86.996^\circ \\ 1.8293 \cdot 10^{-3} \angle 90.137^\circ & 0.8747 \angle 0.4409^\circ \end{bmatrix}$$

# Example

---

Given we're delivering 1000MVA at rated voltage, pf = 0.8 lagging

Determine the sending end voltage and current.

$$V_R \text{ (per phase)} = \frac{765000}{\sqrt{3}} = 441673\angle 0^\circ$$

$$I_R = \left( \frac{1000 \cdot 10^6 \angle 36.87^\circ}{\sqrt{3} \cdot 765000 \angle 0^\circ} \right)^* = 754.7 \angle -36.87^\circ$$

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} 0.8747 \angle 0.4409^\circ & 128.6374 \angle 86.996^\circ \\ 1.8293 \cdot 10^{-3} \angle 90.137^\circ & 0.8747 \angle 0.4409^\circ \end{bmatrix} \cdot \begin{bmatrix} 441673 \angle 0^\circ \\ 754.7 \angle -36.87^\circ \end{bmatrix} = \begin{bmatrix} 455202 \angle 9.8^\circ \\ 673.105 \angle 38.17^\circ \end{bmatrix}$$

$$S_{in} = 3 \cdot (455202 \angle 9.8^\circ)(673.105 \angle -38.17^\circ) = 919.196 \angle -28.37^\circ \text{ MVA}$$

$$S_{in} = 808.798 \text{MW} - j 436.768 \text{MVAR}$$

## Example

---

$$S_{out} = 1000\angle 36.87 \text{ MVA} = 800MW + j600MVAR$$

$$\eta = \frac{P_{out}}{P_{in}} = \frac{800}{808.798} \cdot 100\% = 98.91\%$$

$$|V_S| = 455202 \quad |V_R| = 441763 \quad V_S \text{ is about 3\% larger than } V_R$$

however


$$V_S = AV_R + BI_R \text{ under no-load conditions } I_R = 0$$

$$|V_{R \text{ no-load}}| = \left| \frac{V_S}{A} \right| = \left| \frac{455202}{0.8747} \right| = 520409.28$$

$$V_{REG} = \frac{V_{NL} - V_{FL}}{V_{FL}} \cdot 100\% = \frac{520409.28 - 441763}{441763} \cdot 100\% = 17.8\%$$

# Lumped Parameter Network

---

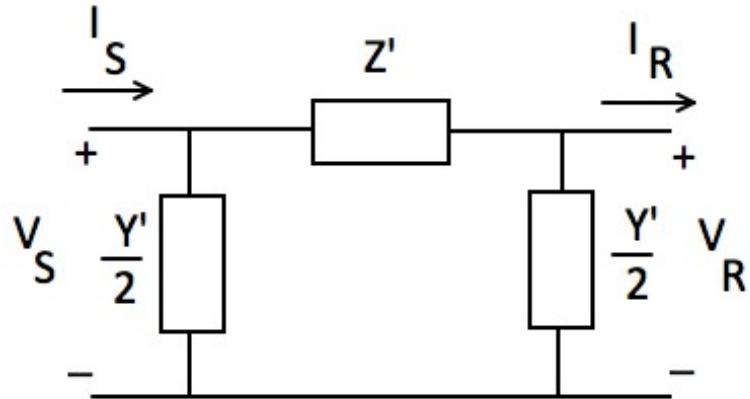

$$V_S = V_R + \left[ V_R \left( \frac{Y'}{2} \right) + I_R \right] Z'$$

$$V_S = \left( 1 + \frac{Z' Y'}{2} \right) V_R + Z' I_R$$

$$V_S = A V_R + B I_R$$



$$I_S = V_S \left( \frac{Y'}{2} \right) + V_R \left( \frac{Y'}{2} \right) + I_R$$

$$I_S = \left( \frac{Y'}{2} \right) \left( 1 + \frac{Z' Y'}{2} \right) V_R + \left( \frac{Y'}{2} \right) Z' I_R + V_R \left( \frac{Y'}{2} \right) + I_R$$

$$I_S = \left( Y' + \frac{Z' Y'^2}{4} \right) V_R + \left( 1 + \frac{Z' Y'}{2} \right) I_R$$

$$I_S = C V_R + D I_R$$

# Lumped Parameter Network

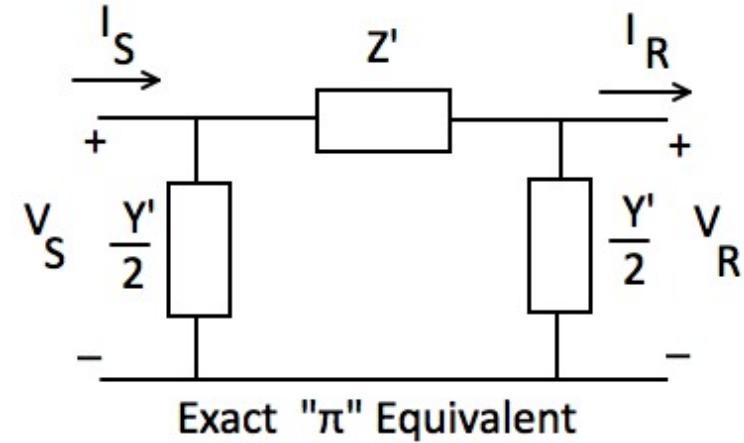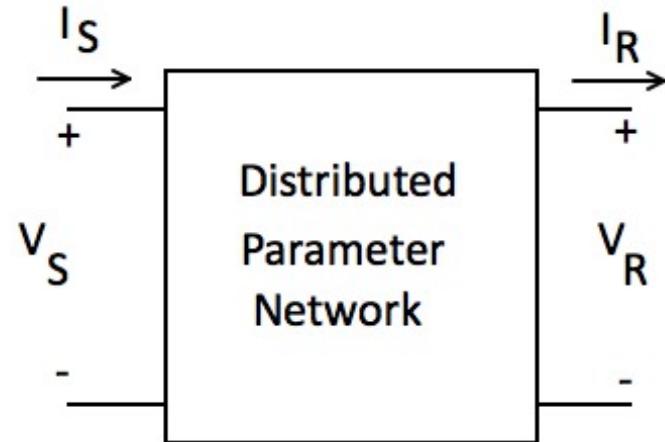

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cosh(\gamma l) & Z_C \cdot \sinh(\gamma l) \\ \frac{1}{Z_C} \sinh(\gamma l) & \cosh(\gamma l) \end{bmatrix}$$

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \left(1 + \frac{Z' Y'}{2}\right) & Z' \\ \left(Y' + \frac{Z' Y'^2}{4}\right) & \left(1 + \frac{Z' Y'}{2}\right) \end{bmatrix}$$

# Lumped Parameter Network

---


$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cosh(\gamma l) & Z_C \cdot \sinh(\gamma l) \\ \frac{1}{Z_C} \sinh(\gamma l) & \cosh(\gamma l) \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \left(1 + \frac{Z' Y'}{2}\right) & Z' \\ \left(Y' + \frac{Z' Y'^2}{4}\right) & \left(1 + \frac{Z' Y'}{2}\right) \end{bmatrix}$$


$$Z' = Z_C \cdot \sinh(\gamma l)$$

$$\left(1 + \frac{Z' Y'}{2}\right) = \cosh(\gamma l) \quad \frac{Z' Y'}{2} = \cosh(\gamma l) - 1$$
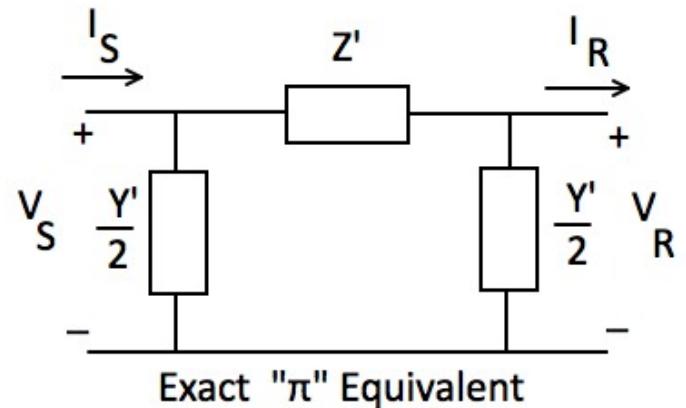
$$\frac{Y'}{2} = \frac{\cosh(\gamma l) - 1}{Z_C \cdot \sinh(\gamma l)} = \frac{1}{Z_C} \tanh\left(\frac{\gamma l}{2}\right)$$



## Returning to our Example

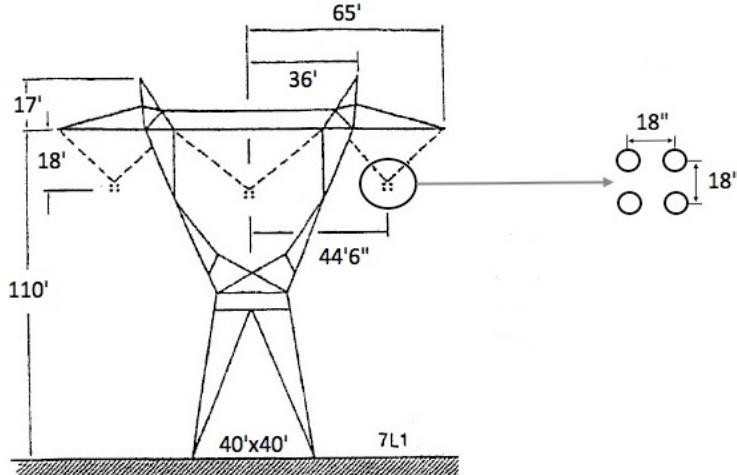

Per Table A4:

Outside Diameter = 1.162" GMR = 0.0391'

$R_{50C\ 60Hz} = 0.1185 \text{ ohms/mile}$

$$Y = 4.77432 \cdot 10^{-6} \angle 90^\circ \Omega/km$$

$$Z = 0.018412 + j0.335235 \Omega/km = 0.33574 \angle 86.859^\circ$$

$$\gamma = \sqrt{ZY} = \sqrt{(0.33574 \angle 86.859^\circ)(4.77432 \cdot 10^{-6} \angle 90^\circ)} = 0.0012661 \angle 88.430^\circ/km$$

$$\gamma l = 0.50643 \angle 88.430^\circ \quad Z_C = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{(0.33574 \angle 86.859^\circ)}{(4.77432 \cdot 10^{-6} \angle 90^\circ)}} = 265.183 \angle -1.571^\circ$$

$$Z' = Z_C \sinh(\gamma l) = 265.183 \angle -1.571^\circ \sinh(0.50644 \angle 88.428^\circ) = 128.637 \angle 86.995^\circ$$

$$\frac{Y'}{2} = \frac{1}{Z_C} \tanh\left(\frac{\gamma l}{2}\right) = \frac{1}{265.183 \angle -1.571^\circ} \tanh\left(\frac{0.50644 \angle 88.428^\circ}{2}\right) = 9.758 \cdot 10^{-4} \angle 89.931^\circ$$


# Lumped Parameter Solution

---

$$Z' = 128.6374 \angle 86.995^\circ \Omega$$

$$\frac{Y'}{2} = 9.758 \cdot 10^{-4} \angle 89.931^\circ S$$
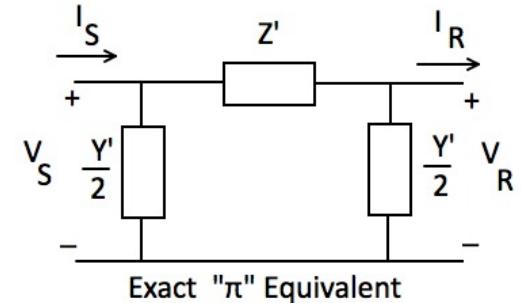
$$V_R \text{ (per phase)} = \frac{765000}{\sqrt{3}} = 441673 \angle 0^\circ$$



$$I_R = \left( \frac{1000 \cdot 10^6 \angle 36.87^\circ}{\sqrt{3} \cdot 765000 \angle 0^\circ} \right)^* = 754.71 \angle -36.87^\circ A$$

$$I_{\frac{Y'}{2}(R)} = 441673 \angle 0^\circ \cdot 9.758 \cdot 10^{-4} \angle 89.931^\circ S = 430.985 \angle 89.931^\circ A$$

$$I_{Z'} = I_R + I_{\frac{Y'}{2}(R)} = 754.7 \angle -36.87^\circ + 430.985 \angle 89.931^\circ = 604.673 \angle -2.070 A$$

$$V_{Z'} = I_{Z'} \cdot Z' = 604.673 \angle -2.070 \cdot 128.6374 \angle 86.995^\circ \Omega = 77783.52 \angle 84.925^\circ V$$

$$V_S = V_{Z'} + V_R = 77783.52 \angle 84.925^\circ + 441673 \angle 0^\circ = 455195.38 \angle 9.80^\circ V$$

$$\begin{aligned} I_S &= V_S \cdot \frac{Y'}{2} + I_{Z'} = 455195.38 \angle 9.80^\circ \cdot 9.758 \cdot 10^{-4} \angle 89.931^\circ + 604.673 \angle -2.070 \\ &= 673.102 \angle 38.167^\circ A \end{aligned}$$

# The Nominal Pi Equivalent Circuit

---

$$Z' = Z_C \sinh(\gamma l) = \sqrt{\frac{Z}{Y}} \sinh\left(\sqrt{ZY} \cdot l\right)$$

$$\sinh(x) = x + \frac{x^3}{3!} + \frac{x^5}{5!} + \frac{x^7}{7!} + \dots$$

$$Z' = \sqrt{\frac{Z}{Y}} \left[ \left( \sqrt{ZY} \cdot l \right) + \frac{\left( \sqrt{ZY} \cdot l \right)^3}{3!} + \frac{\left( \sqrt{ZY} \cdot l \right)^5}{5!} + \dots \right]$$

$$Z' \approx \sqrt{\frac{Z}{Y}} \left( \sqrt{ZY} \cdot l \right) \approx Zl$$

$$Z_{\text{nominal } \pi} = Zl$$

# The Nominal Pi Equivalent Circuit

---

$$\frac{Y'}{2} = \frac{\cosh(\gamma l) - 1}{Z_C \sinh(\gamma l)}$$

$$\cosh(x) = 1 + \frac{x^2}{2!} + \frac{x^4}{4!} + \frac{x^6}{6!} + \dots$$

$$\frac{Y'}{2} = \frac{\left[ 1 + \frac{(\sqrt{ZY} \cdot l)^2}{2!} + \frac{(\sqrt{ZY} \cdot l)^4}{4!} + \dots \right] - 1}{\sqrt{\frac{Z}{Y}} \left[ (\sqrt{ZY} \cdot l) + \frac{(\sqrt{ZY} \cdot l)^3}{3!} + \frac{(\sqrt{ZY} \cdot l)^5}{5!} + \dots \right]}$$

$$\frac{Y'}{2} \approx \frac{\frac{(\sqrt{ZY} \cdot l)^2}{2}}{\sqrt{\frac{Z}{Y}} (\sqrt{ZY} \cdot l)} \approx \frac{\sqrt{ZY} \cdot l}{2 \cdot \sqrt{\frac{Z}{Y}}} \approx \frac{Y \cdot l}{2} = \frac{Y}{2}$$


$$\frac{Y}{2 \text{ nominal } \pi} = \frac{Y \cdot l}{2}$$

# The Nominal Pi Equivalent Circuit

---

$$Z_{\text{nominal } \pi} = Zl$$
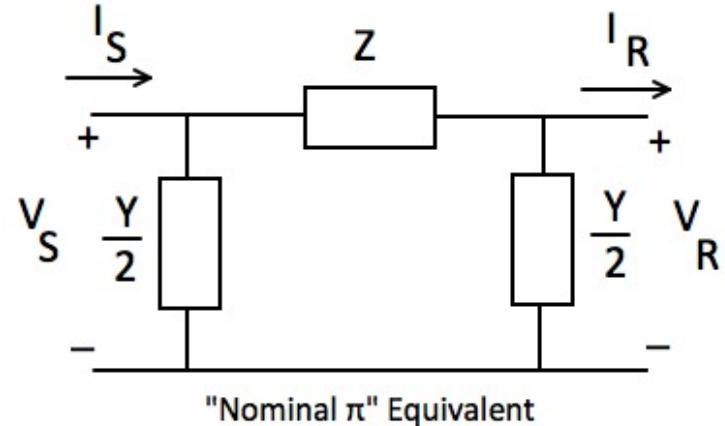
$$\frac{Y}{2}_{\text{nominal } \pi} = \frac{Y \cdot l}{2}$$



$$Zl = 0.33574 \angle 86.995^\circ \cdot 400 = 134.296 \angle 86.995^\circ = Z_{\text{nominal } \pi}$$

$$\frac{Y \cdot l}{2} = \frac{4.77432 \cdot 10^{-6} \angle 90^\circ \cdot 400}{2} = 9.5486 \cdot 10^{-4} \angle 90^\circ = \frac{Y}{2}_{\text{nominal } \pi}$$

Recall the exact parameters:


$$Z' = Z_C \sinh(\gamma l) = 265.183 \angle -1.571^\circ \sinh(0.50644 \angle 88.428^\circ) = 128.637 \angle 86.995^\circ$$

$$\frac{Y'}{2} = \frac{1}{Z_C} \tanh\left(\frac{\gamma l}{2}\right) = \frac{1}{265.183 \angle -1.571^\circ} \tanh\left(\frac{0.50644 \angle 88.428^\circ}{2}\right) = 9.758 \cdot 10^{-4} \angle 89.931^\circ$$
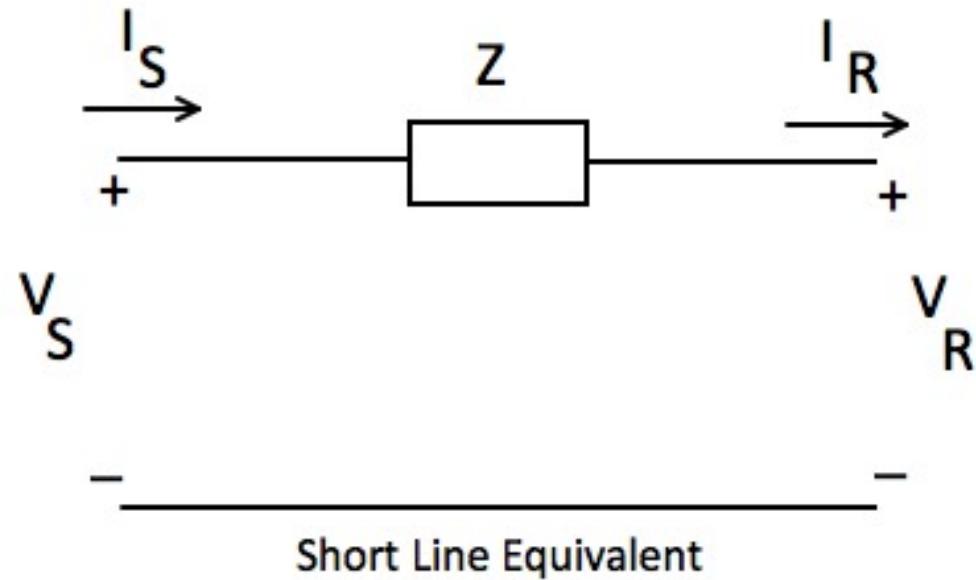
# Short Line Approximation

---

Since the shunt admittance is normally quite small, as the line length gets small  $Yl/2$  becomes negligible and  $Y/2 \Rightarrow 0$ . If the admittance approaches zero, the impedance approaches infinity. The short line equivalent circuit is shown below.



# Three Lumped Parameter Line Models

---

Exact  $\pi$

$$Z' = Z_C \sinh(\gamma l)$$
$$\frac{Y'}{2} = \frac{1}{Z_C} \tanh\left(\frac{\gamma l}{2}\right)$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}$$

$$\begin{bmatrix} \cosh(\gamma l) & Z_C \cdot \sinh(\gamma l) \\ \frac{1}{Z_C} \sinh(\gamma l) & \cosh(\gamma l) \end{bmatrix}$$

Nominal  $\pi$

$$Z = Zl$$
$$\frac{Y}{2} = \frac{Yl}{2}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}$$

$$\begin{bmatrix} \left(1 + \frac{ZY}{2}\right) & Z \\ \left(Y + \frac{ZY^2}{4}\right) & \left(1 + \frac{ZY}{2}\right) \end{bmatrix}$$

Short Line

$$Z = Zl$$
$$\frac{Y}{2} = 0$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}$$

$$\begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix}$$

## How do I know what to use??

---



Line Length	Appropriate Model
80km or less	Short line
80km – 250km	Nominal $\pi$
greater than 250 km	Exact $\pi$

Or – whatever I tell you to use !!!

Table 5.1 pg 258

# Comparison Calculations

---

400 km long line

	Exact	Nominal	Short
A=D	0.8747∠44.07	0.8720∠46.15	1.0000
Z' (Z)=B	128.6∠87.00	134.3∠86.86	134.3∠86.86
C	1.829x10 <sup>-3</sup> ∠90.14	1.665x10 <sup>-3</sup> ∠90.46	0.0000
Y'/2 (Y/2)	9.757x10 <sup>-4</sup> ∠89.93	9.548x10 <sup>-4</sup> ∠90.00	0.0000
V <sub>s</sub>	455.2 kV ∠9.80	457.5 kV ∠10.2	512.8 kV ∠8.7
I <sub>s</sub>	673.0∠38.16	627.0∠33.36	754.7∠-36.87

100 km long line

	Exact	Nominal	Short
A=D	0.9920∠.0253	0.9920∠.0254	1.0000
Z' (Z)=B	33.49∠86.87	33.58∠86.86	33.58∠86.86
C	4.761x10 <sup>-4</sup> ∠90.01	4.736x10 <sup>-4</sup> ∠90.03	0.0000
Y'/2 (Y/2)	2.390x10 <sup>-4</sup> ∠90.00	2.387x10 <sup>-4</sup> ∠90.00	0.0000
V <sub>s</sub>	454.8 kV ∠2.464	454.9 kV ∠2.470	458.4 kV ∠2.427
I <sub>s</sub>	644.9∠-21.72	645.2∠-21.81	754.7∠-36.87

	25 km long line		
	Exact	Nominal	Short
A=D	0.9995∠.00157	1.0000∠.0034	1.0000
Z' (Z)=B	8.392∠86.86	8.394∠86.86	8.394∠86.86
C	1.193x10 <sup>-4</sup> ∠90.00	1.194x10 <sup>-4</sup> ∠90.00	0.0000
Y'/2 (Y/2)	5.968x10 <sup>-5</sup> ∠90.00	5.968x10 <sup>-5</sup> ∠90.00	0.0000
V <sub>s</sub>	445.6 kV ∠.625	445.7 kV ∠.627	445.8 kV ∠.624
I <sub>s</sub>	723.9∠-33.5	724.3∠-33.5	754.7∠-36.87

765 kV line:

$$z = .33575∠86.86 \Omega/\text{km}$$

$$y = 4.7740 \times 10^{-6}∠90.00 \text{ S/km}$$

$$Z_C = 265.2∠-1.572 \Omega$$

$$\gamma = 1.266 \times 10^{-3}∠88.43 / \text{km}$$

$$V_R = 441,673 \text{ V/phase}$$

$$I_R = 754.7∠-36.87 \text{ A}$$

## Lossless Lines

---

$$Z = 0.18396 + j0.33524 \Omega/km$$

$$Y = j4.77432 \cdot 10^{-6} S/km$$

if we neglect  $R$

$$Z = j0.33524 \Omega/km$$

$$Z_C = \sqrt{\frac{Z}{Y}} = 264.986\Omega \quad \text{"Surge Impedance" of a lossless line (purely real)}$$

$$\gamma = \sqrt{ZY} = j0.0012649 /km = \alpha + j\beta \quad (\alpha = 0 \text{ purely imaginary})$$

$$\cosh(x) = \frac{e^x + e^{-x}}{2} \quad \cosh(j\beta) = \frac{e^{j\beta} + e^{-j\beta}}{2} = \cos(\beta)$$

$$\sinh(x) = \frac{e^x - e^{-x}}{2} \quad \sinh(j\beta) = \frac{e^{j\beta} - e^{-j\beta}}{2} = j \sin(\beta)$$

# Lossless Lines

---

$$\begin{bmatrix} A_{(x)} & B_{(x)} \\ C_{(x)} & D_{(x)} \end{bmatrix} = \begin{bmatrix} \cos(0.0012649 \cdot x) & j264.986 \sin(0.0012649 \cdot x) \\ j\frac{1}{264.986} \sin(0.0012649 \cdot x) & \cos(0.0012649 \cdot x) \end{bmatrix}$$

but 1 radian = 57.296°

$$\begin{bmatrix} A_{(x)} & B_{(x)} \\ C_{(x)} & D_{(x)} \end{bmatrix} = \begin{bmatrix} \cos(0.072473 \cdot x^\circ) & j264.986 \sin(0.072473 \cdot x^\circ) \\ j\frac{1}{264.986} \sin(0.072473 \cdot x^\circ) & \cos(0.072473 \cdot x^\circ) \end{bmatrix}$$

converting to p.u.  $V_{base} = 765kV$  and  $S_{base} = 1000MVA$

$$Z_{base} = \frac{(765 \cdot 10^3)^2}{1000 \cdot 10^6} = 585.225$$

$$\begin{bmatrix} A_{(x)} & B_{(x)} \\ C_{(x)} & D_{(x)} \end{bmatrix} = \begin{bmatrix} \cos(0.072473 \cdot x^\circ) & j0.45279 \sin(0.072473 \cdot x^\circ) \\ j2.20851 \sin(0.072473 \cdot x^\circ) & \cos(0.072473 \cdot x^\circ) \end{bmatrix}$$

## Lossless Line

---

$$V_{(x)} = A_{(x)} \cdot V_R + B_{(x)} \cdot I_R$$

$$V_{(x)} = \cos(0.072473 \cdot x^\circ) \cdot V_R + j264.986 \sin(0.072473 \cdot x^\circ) \cdot I_R$$

if we terminate the line with a surge impedance load

$$I_R = \frac{V_R}{Z_C}$$


$$V_{(x)} = \cos(0.072473 \cdot x^\circ) \cdot V_R + j \sin(0.072473 \cdot x^\circ) \cdot V_R$$

$$V_{(x)} = [\cos(0.072473 \cdot x^\circ) + j \sin(0.072473 \cdot x^\circ)] \cdot V_R$$

$$V_{(x)} = (1 \angle 0.072473 \cdot x^\circ) \cdot V_R$$

# Lossless Line

---

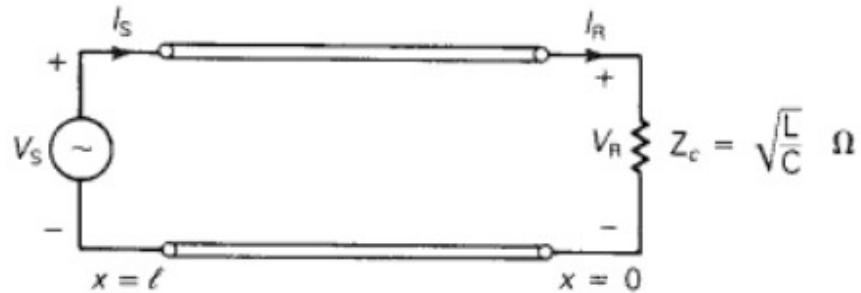

$$V_{(x)} = \cos(0.072473 \cdot x^\circ) \cdot V_R + j Z_C \sin(0.072473 \cdot x^\circ) \cdot I_R$$

$$I_{(x)} = j \frac{1}{Z_C} \sin(0.072473 \cdot x^\circ) \cdot V_R + \cos(0.072473 \cdot x^\circ) \cdot I_R$$

under surge impedance loading,  $I_R = \frac{V_R}{Z_C}$

$$V_{(x)} = \cos(0.072473 \cdot x^\circ) \cdot V_R + j \sin(0.072473 \cdot x^\circ) \cdot V_R$$

$$V_{(x)} = (1 \angle 0.072473 \cdot x^\circ) V_R$$


$$I_{(x)} = j \frac{1}{Z_C} \sin(0.072473 \cdot x^\circ) \cdot V_R + \cos(0.072473 \cdot x^\circ) \cdot \frac{V_R}{Z_C}$$

$$I_{(x)} = (1 \angle 0.072473 \cdot x^\circ) V_R$$

$$S_{(x)} = V_{(x)} \cdot (I_{(x)})^* = \frac{|V_R|^2}{Z_C}$$

The real power flow is constant along the length of the line.

The reactive power flow is zero.

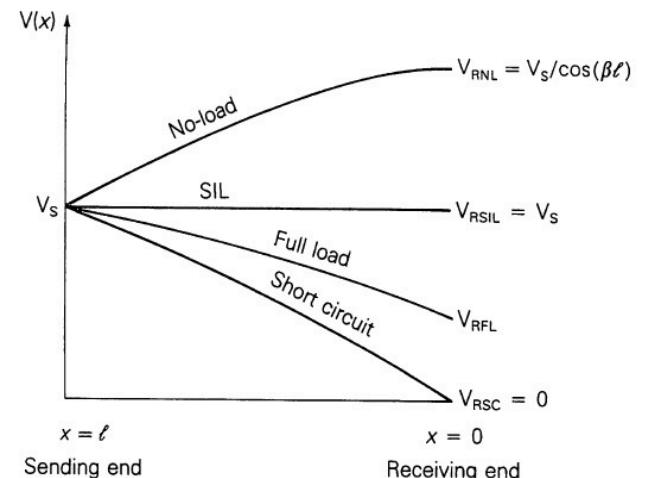

# Wavelength

---

$$V_{(x)} = (1\angle 0.072473 \cdot x^\circ) \cdot V_R$$

$$V_{(x)} = (1\angle 0.072473 \cdot (400)^\circ) \cdot V_R$$



$$V_{(x)} = (1\angle 28.99^\circ) \cdot V_R$$

Wavelength is defined as the distance required to change the phase of the voltage or current by  $360^\circ$ .

$$0.072473 \cdot \lambda^\circ = 360^\circ \quad \lambda = 4,968 \text{ km} = 3088 \text{ miles}$$

Typical transmission lines are only a small fraction of a wavelength.

# Steady State Stability Limit

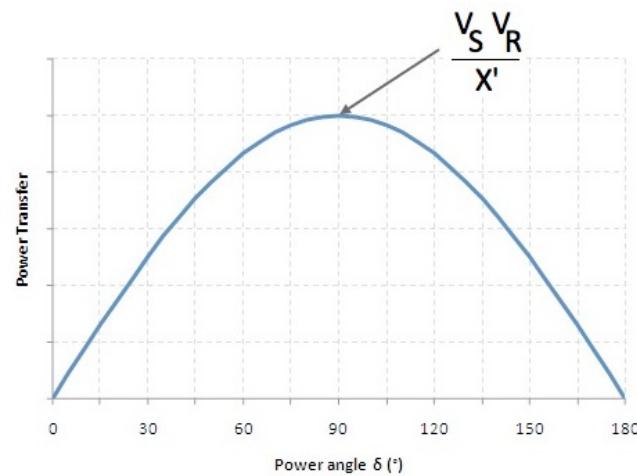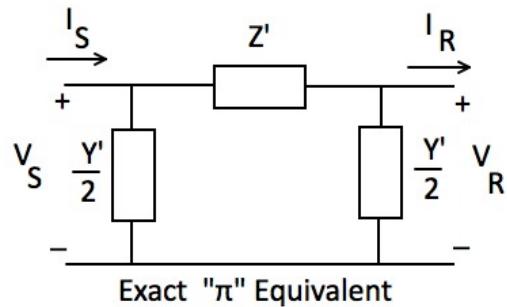

$$I_R = \frac{V_S - V_R}{Z'} - \frac{Y'}{2} \cdot V_R$$

$$S_R = V_R \cdot I_R^* = V_R \cdot \left( \frac{V_S - V_R}{Z'} - \frac{Y'}{2} \cdot V_R \right)^*$$

$$V_R = V_R \angle 0^\circ \quad V_S = V_S \angle \delta^\circ \quad Z' = jX' \text{ and } Y' = j\omega C' l$$

$$S_R = V_R \left( \frac{V_S \angle \delta - V_R}{jX'} \right)^* + \frac{j\omega C' l}{2} V_R^2$$

$$S_R = V_R \left( \frac{V_S \angle -\delta - V_R}{-jX'} \right) + \frac{j\omega C' l}{2} V_R^2$$

$$S_R = \frac{V_R V_S \angle 90 - \delta}{X'} - j \frac{V_R^2}{X'} + \frac{j\omega C' l}{2} V_R^2$$


$$S_R = P_R + jQ_R$$

$$P_R = \frac{|V_R| \cdot |V_S|}{|X'|} \cos(90 - \delta^\circ) = \frac{|V_R| \cdot |V_S|}{|X'|} \sin \delta$$

# Steady State Stability Limit

---

$$P_R = \frac{|V_R| \cdot |V_S|}{|X'|} \sin \delta$$

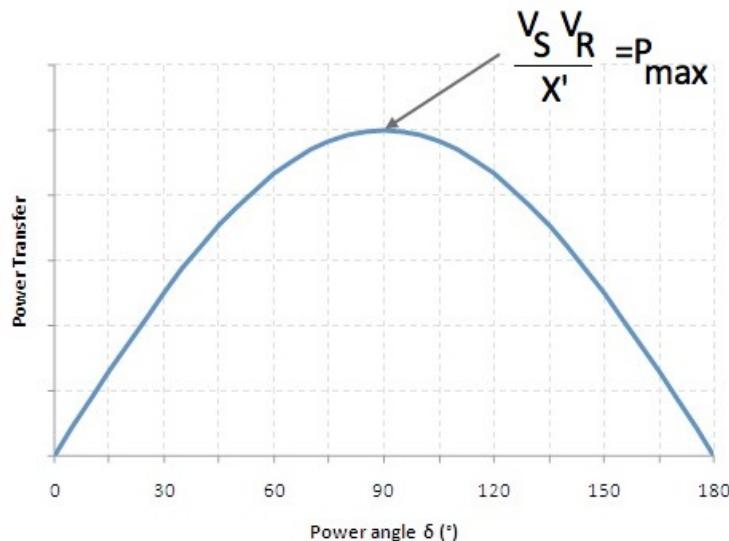

When  $\delta = 90^\circ$ ,  $\sin \delta = 1.0$  and  $P_R = P_{R\ MAX}$

$P_{R\ MAX}$  = the “theoretical steady state stability limit” of a lossless line.

If one were to try and exceed this limit the generators at the sending end of the line would lose synchronization with the machines on the receiving end of the line and that would be really really bad!

# Exceeding The Stability Limit

---



# Exceeding the Stability Limit

---



# Exceeding the Stability Limit

---



# Steady State Stability Limit

We could do the same analysis using the ABCD parameters:


$$V_S = AV_R + BI_R \quad I_R = \frac{V_S - AV_R}{B}$$

$$S_R = V_R \cdot (I_R)^*$$

$$P_R = \frac{|V_R| \cdot |V_S|}{B} \sin \delta = \frac{|V_R| \cdot |V_S|}{Z_C \sin \beta l} \sin \delta$$

$$P_R = \frac{|V_R|}{V_{Rated}} \cdot \frac{|V_S|}{V_{Rated}} \cdot \frac{(V_{Rated})^2}{Z_C} \cdot \frac{\sin \delta}{\sin \beta l}$$
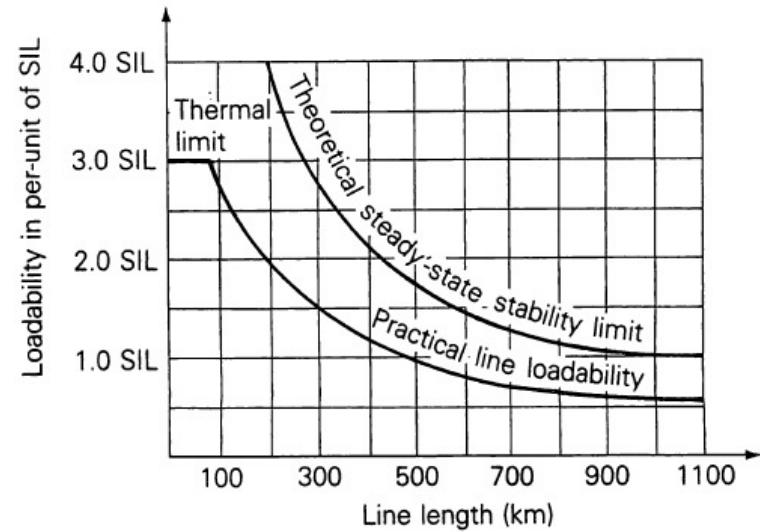
$$P_R = V_{R(pu)} \cdot V_{S(pu)} \cdot SIL \cdot \frac{\sin \delta}{\sin \beta l}$$



The result shows the receiving end power is proportional to the square of the voltage i.e., a doubling of voltage produces a fourfold increase in maximum power.

The result also shows the receiving end power is inversely proportional to line length.

# Line Loadability

Voltage kV	Zc(range) ohms	Zc(used) ohms	S.I.L (MW)	400 km line		200 km line	
				P(max) (MW)	P(limit) (MW)	P(max) (MW)	P(limit) (MW)
230	365-395	380	139	289	166	559	321
345	280-366	320	372	772	443	1496	858
500	233-294	260	961	1995	1144	3864	2216
765	254-266	260	2,250	4671	2679	9047	5190

5,000 km wavelength used in calculations

$$P_{R \ MAX} = \frac{V_R V_S}{Z_C \sin \beta l} = \frac{V_R V_S}{Z_C \sin \frac{2\pi l}{\lambda}}$$

$$P_{R \ MAX} = \frac{V_R V_S}{Z_C \sin \left( \frac{360^\circ}{5000 \text{km}} \right) 400 \text{km}}$$

$$P_{R \ MAX} = \frac{(230 \cdot 10^3)^2}{380(0.4818)} = 289 \text{MW}$$



Volts	Lines Required
230kV	16 (15.06)
345kV	6 (5.64)
500kV	3 (2.18)
765kV	1

$$P_{R \ LIMIT} = P_{R \ MAX} \sin 35^\circ = 166 \text{MW}$$

# Receiving End Power

---

$$V_S = AV_R + BI_R \quad I_R = \frac{V_S - AV_R}{B}$$

$$I_S = CV_R + DI_R$$

$$S_R = V_R \cdot (I_R)^*$$

$$V_R = |V_R| \angle 0^\circ \quad V_S = |V_S| \angle \delta \quad B = |B| \angle \beta \quad A = |A| \angle \alpha$$

$$S_R = \frac{|V_R| \cdot |V_S|}{|B|} \angle \beta - \delta - \frac{|V_R|^2 |A|}{|B|} \angle \beta - \alpha$$

$$S_R = \frac{|V_R| \cdot |V_S|}{|B|} \angle \beta - \delta + \frac{|V_R|^2 |A|}{|B|} \angle \beta - \alpha - 180$$


# Receiving End Circle Diagram

$$S_R = \frac{|V_R| \cdot |V_S|}{|B|} \angle \beta - \delta + \frac{|V_R|^2 |A|}{|B|} \angle \beta - \alpha - 180$$

$$S_R = P_R + jQ_R$$

$$S_R = \frac{|V_R|^2 |A|}{|B|} \angle \beta - \alpha - 180 + \frac{|V_R| \cdot |V_S|}{|B|} \angle \beta - \delta$$

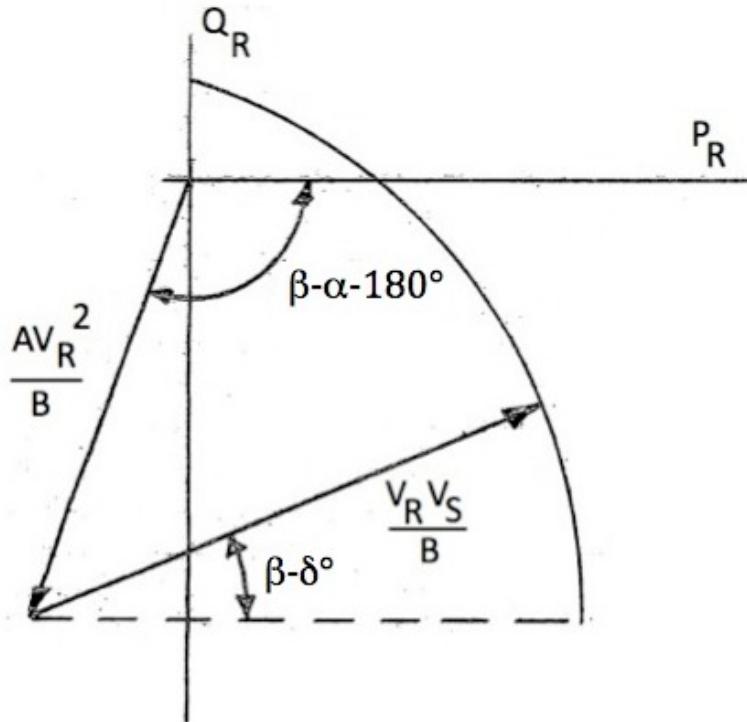fixed                          varies with  $\delta$



## Example

---

400km 765kV line  $B = 128.6 \angle 86.99^\circ$   $A = 0.8747 \angle 0.4412^\circ$

$S_{\text{base}} = 1000 \text{MVA}$   $V_{\text{base}} = 765 \text{kV}$   $Z_{\text{base}} = 585.2 \Omega$

$B_{\text{p.u.}} = 0.219745 \angle 86.99^\circ$   $A_{\text{p.u.}} = 0.8747 \angle 0.4412^\circ$

The magnitude of  $V_R = V_S = 1.0_{\text{p.u.}}$

$$S_R = \frac{|V_R|^2 |A|}{|B|} \angle \beta - \alpha - 180 + \frac{|V_R| \cdot |V_S|}{|B|} \angle \beta - \delta$$

$$S_R = \frac{1^2 \cdot 0.8747}{0.219745} \angle 86.99 - 0.4412 - 180 + \frac{1 \cdot 1}{0.219745} \angle 86.99 - \delta$$

$$S_R = 3.980531 \angle -93.46 + 4.550739 \angle 86.99 - \delta$$

# Receiving End Circle Diagram

---

$$S_R = 3.980531 \angle -93.46 + 4.550739 \angle 86.99 - \delta$$

$$P_R = 3.98 \cos(-93.46) + 4.55 \cos(86.99 - \delta)$$

$$P_R = -0.24 + 4.55 \cos(86.99 - \delta)$$

$$Q_R = 3.98 \sin(-93.46) + 4.55 \sin(86.99 - \delta)$$

$$Q_R = -3.97 + 4.55 \sin(86.99 - \delta)$$

When will  $P_R = P_{R \text{ MAX}}$  ???


$$\delta = 86.99 \text{ and } \cos(0^\circ) = 1$$

$$P_{R \text{ MAX}} = -0.24 + 4.55 \cos(0^\circ) = 4.31 \text{ p.u.} = 4310.5 \text{ MW}$$

$$Q_{R \text{ MAX}} = -3.97 + 4.55 \sin(0^\circ) = -3.97 \text{ p.u.} = 3972.6 \text{ MVAR}$$

$$p.f. = P/S = 0.736 \text{ leading}$$
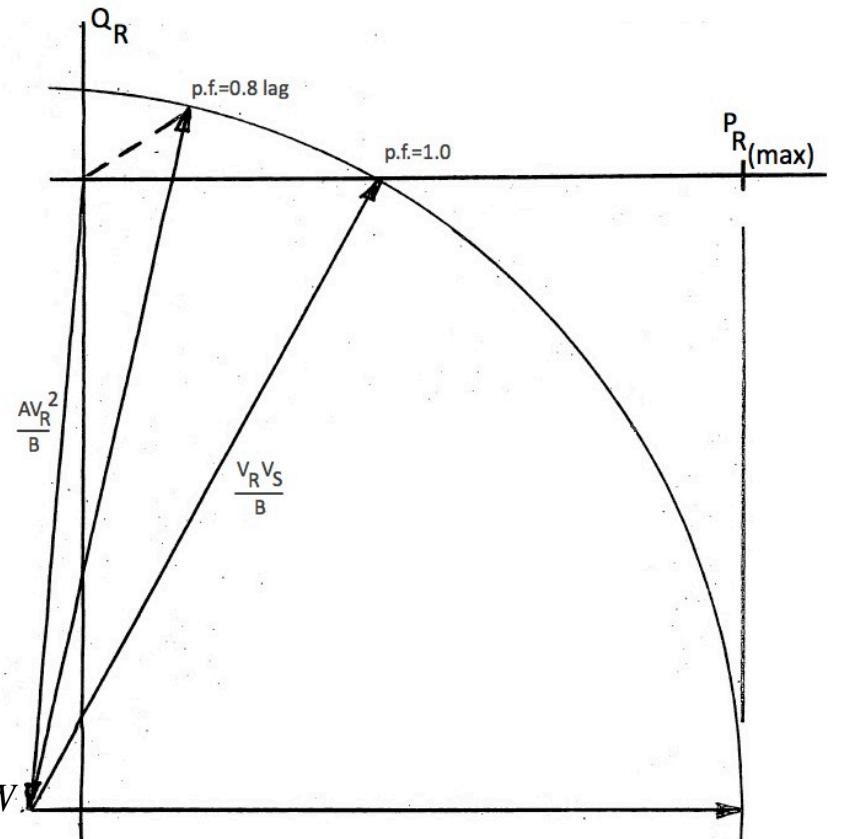
$$\text{Recall from the lossless calculations : } P_{R \text{ MAX}} = 4558 \text{ MW}$$



# Receiving End Circle Diagram

$P_R = P_{R\ MAX}$  when  $\delta = 86.99^\circ$  and  $\cos(0^\circ) = 1$

This is too close to the limit of  $\delta = 90^\circ$


What is the receiving end power when  $\delta = 35^\circ$  ?

$$S_R = 3.980531 \angle -93.46 + 4.550739 \angle 86.99 - \delta$$

$$P_R = 3.98 \cos(-93.46) + 4.55 \cos(86.99 - 35)$$

$$P_R = -0.24 + 2.80 = 2.562 \text{ p.u.} = 2562 \text{ MW}$$

$$P_{R\ lossless} = 2598 \text{ MW}$$

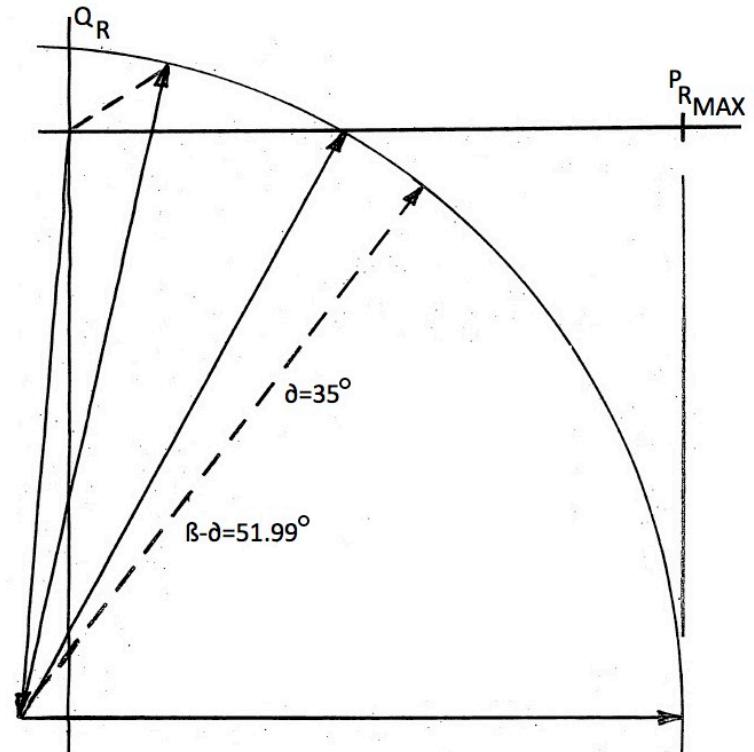

$$Q_R = 3.98 \sin(-93.46) + 4.55 \sin(86.99 - 35)$$

$$Q_R = -3.97 + 3.58 = -0.3877 \text{ p.u.} = 387.7 \text{ MVAR}$$

# Receiving End Circle Diagram

How much power can we deliver at unity power factor?

When p.f. = 1.0  $Q_R = 0$  VARs

$$S_R = 3.980531\angle -93.46 + 4.550739\angle 86.99 - \delta$$


$$Q_R = 3.98 \sin(-93.46) + 4.55 \sin(86.99 - \delta) = 0$$

$$(86.99 - \delta) = \sin^{-1}\left(\frac{-3.98 \sin(-93.46)}{4.55}\right) = 60.8^\circ$$

$$\delta = 26.2^\circ$$

$$P_R = 3.98 \cos(-93.46) + 4.55 \cos(86.99 - 26.2)$$
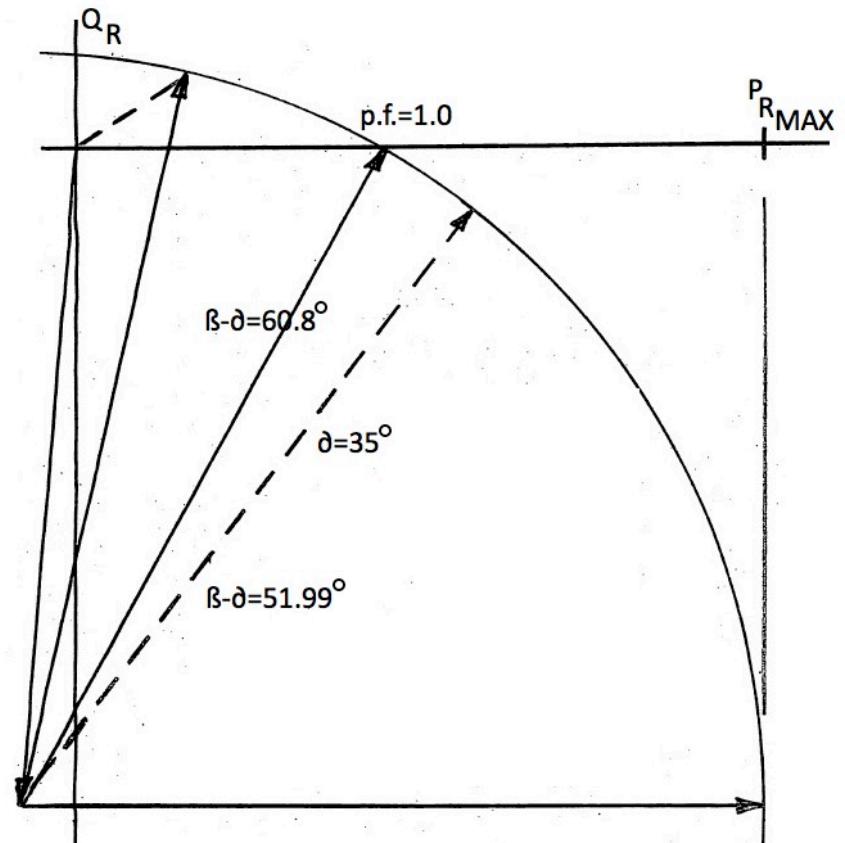
$$P_R = -0.24 + 2.22 = 1.983 \text{ p.u.} = 1983 \text{ MW}$$



# Receiving End Circle Diagram

What is the receiving end power at p.f. = 0.8 lagging?

$$p.f. = \frac{P}{S} \quad S = \frac{P}{p.f.} = \frac{P}{.8}$$

$$Q = \sqrt{S^2 - P^2} = \sqrt{\frac{P^2}{.64} - P^2} = 0.75P$$

$$Q_R = 0.75P_R = 3.98 \sin(-93.46) + 4.55 \sin(86.99 - \delta)$$

$$P_R = 3.98 \cos(-93.46) + 4.55 \cos(86.99 - \delta)$$

or  
 $0.75X = 3.98 \sin(-93.46) + 4.55 \sin(86.99 - Y)$  and  
 $X = 3.98 \cos(-93.46) + 4.55 \cos(86.99 - Y), \{X, Y\}$

$$x = -4.77 \quad y = -4768.1 \quad \text{or} \quad x = -4.77 \quad y = -88.06 \quad \text{or}$$

$$x = -4.77 \quad y = 271.94 \quad \text{or} \quad x = -4.77 \quad y = 5671.94 \quad \text{or}$$


$$x = 0.652 \quad y = -2871.7 \quad \text{or} \quad x = 0.652 \quad y = 8.297 \quad \text{or}$$

$$x = 0.652 \quad y = 368.30$$

$$P_R = 0.652 \text{ p.u.} = 652 \text{ MW}$$

$$Q_R = 0.75P_R = 0.489 \text{ p.u.} = 489 \text{ VAR}$$
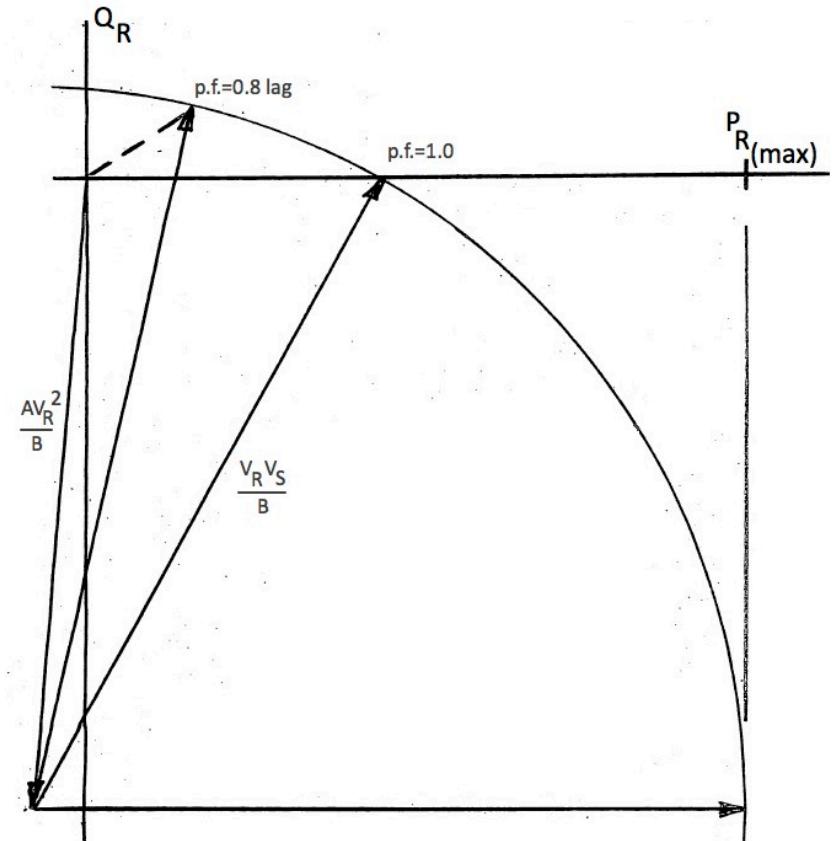
$$Q_R = 3.98 \sin(-93.46) + 4.55 \sin(86.99 - 8.297) = 0.489 \text{ check!}$$



# Receiving End Power - ABCD Parameters

	Exact	Per Unit
A = D	$0.8747\angle 0.4412^\circ$	$0.8747\angle 0.4412^\circ$
Z' = B	$128.6\angle 86.99^\circ$	$0.219745\angle 86.99^\circ$
C	$1.829 \times 10^{-3}\angle 90.14^\circ$	$1.0704\angle 90.14^\circ$
Y'/2	$9.757 \times 10^{-4}\angle 89.93^\circ$	$0.571004\angle 89.93^\circ$
V <sub>base</sub> = 765kV	S <sub>base</sub> = 1000MVA	Z <sub>base</sub> = 585.225
	Length = 400km	

765 kV line:  
 $z = .33575\angle 86.86 \Omega/\text{km}$   
 $y = 4.7740 \times 10^{-6}\angle 90.00 \text{ S/km}$   
 $Z_c = 265.2\angle -1.572 \Omega$   
 $\gamma = 1.266 \times 10^{-3}\angle 88.43^\circ / \text{km}$


$$S_R = \frac{|V_R|^2 |A|}{|B|} \angle \beta - \alpha - 180 + \frac{|V_R| \cdot |V_S|}{|B|} \angle \beta - \delta$$

$$S_R = \frac{0.95^2 \cdot 0.8747}{0.219745} \angle 86.99 - 0.4412 - 180 + \frac{0.95 \cdot 1.05}{0.219745} \angle 86.99 - \delta$$



$$S_R = 3.59242 \angle -93.451 + 4.53935 \angle 86.99 - \delta$$

$$V_S \angle \delta = 0.8747 \angle 0.4412^\circ \cdot 0.95 \angle 0^\circ + 0.219745 \angle 86.99^\circ \cdot I_R \angle -36.87^\circ$$

$$V_S \angle \delta = 0.830965 \angle 0.4412^\circ + 0.219745 |I_R| \angle 50.12^\circ$$

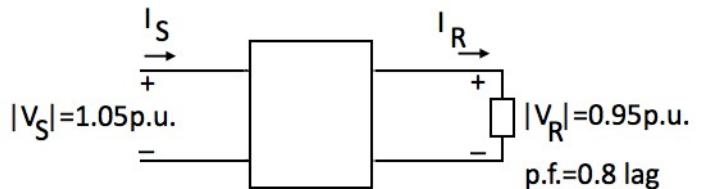

# Receiving End Circle Diagram

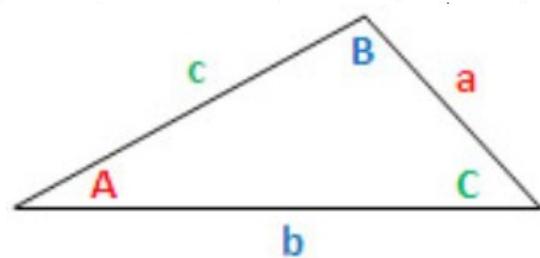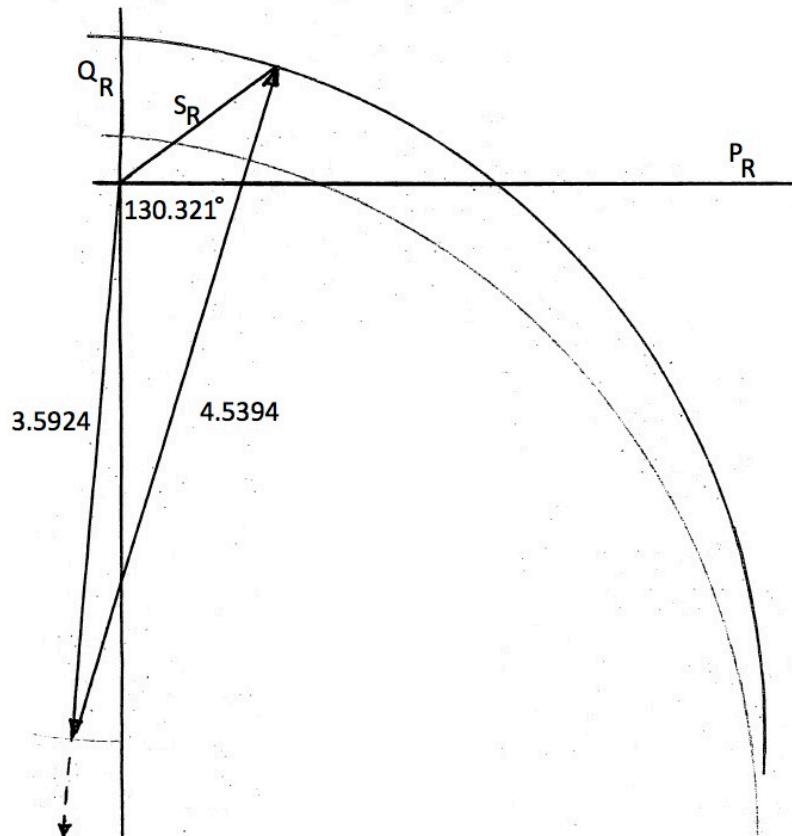

$$S_R = 3.59242\angle -93.451 + 4.53935\angle 86.99 - \delta$$

Applying the Law of Cosines

$$4.53935^2 = 3.59242^2 + |S_R|^2 - 2 \cdot |S_R| \cdot 3.59242 \cos(130.312)$$

Using cSolve

$$x = -5.9458 \quad or \quad x = 1.2953$$

$$P_R = .8 \cdot S_R = 1.0362 \text{ p.u.} = 1036.2 \text{ MW}$$

$$I_R = \left( \frac{S_R}{V_R} \right)^* = \left( \frac{1.2953 \angle 36.87^\circ}{0.95 \angle 0^\circ} \right)^* = 1.3635 \angle -36.87^\circ$$

$$a^2 = b^2 + c^2 - 2bc \cos A$$


$$b^2 = a^2 + c^2 - 2ac \cos B$$

$$c^2 = a^2 + b^2 - 2ab \cos C$$
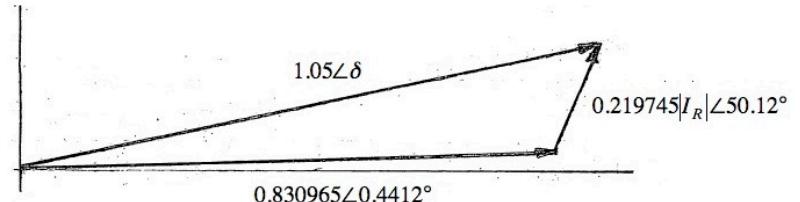
# Receiving End Power - ABCD Parameters

---

$$V_S \angle \delta = 0.8747 \angle 0.4412^\circ \cdot 0.95 \angle 0^\circ + 0.219745 \angle 86.99^\circ \cdot I_R \angle -36.87^\circ$$



$$V_S \angle \delta = 0.830965 \angle 0.4412^\circ + 0.219745|I_R| \angle 50.12^\circ$$

$$1.05\angle \delta = 0.830965 \angle 0.4412^\circ + 0.219745|I_R| \angle 50.12^\circ$$

$$1.05\angle \delta - 0.4412^\circ = 0.830965 \angle 0.4412^\circ - 0.4412^\circ + 0.219745|I_R| \angle 50.12^\circ - 0.4412^\circ$$


$$1.05\angle \delta - 0.4412^\circ = 0.830965 \angle 0^\circ + 0.219745|I_R| \angle 49.68^\circ$$

$$1.05^2 = 0.830965^2 + (0.219745|I_R|)^2 - 2 \cdot 0.219745|I_R| \cdot 0.830965 \cos(130.32)$$

$$x = -6.2572 \quad or \quad x = 1.3636$$

$$S_R = V_R \cdot I_R^* = 0.95 \angle 0^\circ \cdot 1.3636 \angle 36.87^\circ = 1.29542 \angle 36.87^\circ$$

$$P_R = p.f. |S_R| = .8 \cdot 1.29542 = 1.0363 \text{ p.u.} = 1036.3 \text{ MW}$$

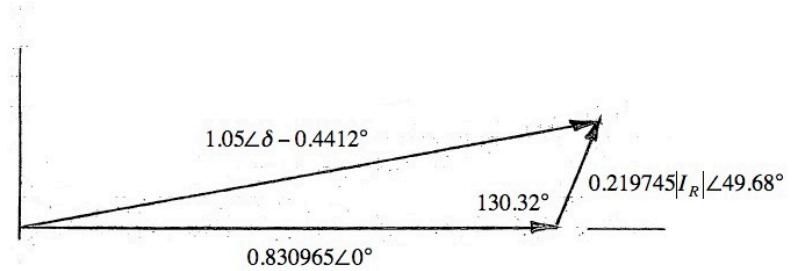

# Voltage Regulation

---

$$V_S = AV_R + BI_R$$


but at no-load  $I_R = 0A$

$$V_S = AV_R \quad |V_R| = \frac{|V_S|}{|A|}$$

for our 765kV, 400km line  $|A| = .8747$


$$V_R = \frac{1.05}{0.8747} = 1.20 \text{ p.u.} \quad 1.2 \cdot 765\text{kV} = 918\text{kV}$$
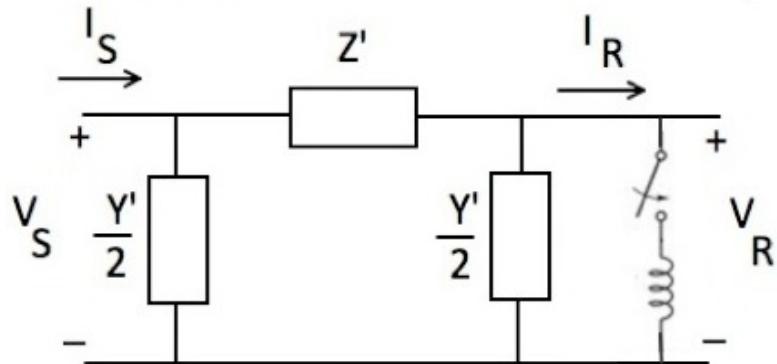
$$V_{REG} = \frac{\frac{1.05}{0.8747} - 1.0}{1.0} \cdot 100\% = 20.04\%$$



# The Inductor as a Two Port

---

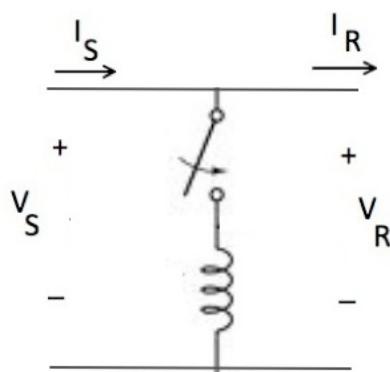

$$V_S = V_R \quad I_S = \frac{V_R}{jX_L} + I_R$$

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ \frac{1}{jX_L} & 1 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \cdot \begin{bmatrix} 1 & 0 \\ \frac{1}{jX_L} & 1 \end{bmatrix}$$

$$A = A_1 \cdot 1 + B_1 \cdot \frac{1}{jX_L} = 0.8747 \angle 0.4412^\circ + 0.219745 \angle 86.99^\circ \cdot \frac{1}{X_L} \angle -90^\circ$$

$$A = 0.8747 \angle 0.4412 + \frac{0.219745}{X_L} \angle -3.01$$

$$|1.0| = 0.8747 \angle 0.4412 + \frac{0.219745}{X_L} \angle -3.01 \quad X_L = 1.751 \text{ p.u.}$$

$$|V_R|_{no\ load} = \frac{|V_S|}{|A|} = \frac{1.05}{1} = 1.05$$

# Shunt Compensation

---

We may also determine  $X_L$  through power considerations:

if  $X_L$  is chosen properly  $|A| = 1.0 \Rightarrow V_{R(\text{no load})} = V_S$

$$S_R = \frac{|V_R|^2 |A|}{|B|} \angle \beta - \alpha - 180 + \frac{|V_R| \cdot |V_S|}{|B|} \angle \beta - \delta$$

$$S_R = \frac{1.05^2 \cdot 0.8747}{0.219745} \angle 86.99 - 0.4412 - 180 + \frac{1.05 \cdot 1.05}{0.219745} \angle 86.99 - \delta$$

$$S_R = 4.385526 \angle -93.45^\circ + 5.017179 \angle 86.99 - \delta^\circ$$


$$P_R = 0$$

$$0 = 4.385526 \cos \angle -93.45^\circ + 5.017179 \cos \angle 86.99 - \delta^\circ$$

$$\angle 86.99 - \delta^\circ = \frac{4.385526 \cos \angle -93.45^\circ}{5.017179} = 86.9827$$

$$Q_R = 4.385526 \sin \angle -93.45^\circ + 5.017179 \sin \angle 86.9827 = 0.62952$$
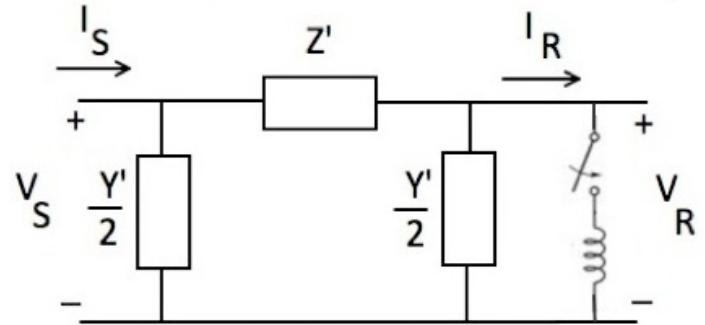
$$Q_R = \frac{V_R^2}{X_L} \Rightarrow X_L = \frac{1.05^2}{0.62952} = 1.75097 \text{ p.u.}$$



# Shunt Compensation


---



500kV 40MVAR Shunt Reactor Bank
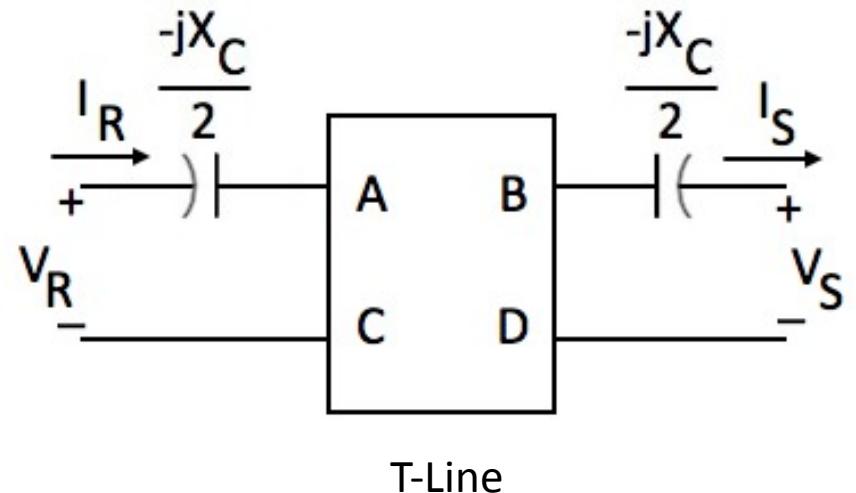
# Series Compensation

Series capacitors can be employed on long transmission lines to increase loadability. They work by reducing the total series reactance of the line. The compensation is expressed in the percent of the inductive reactance that is cancelled by the capacitors. Typically half the compensation is placed on each end of the line.



For out 765kV, 400km line

$$Z' = 0.011539 + j0.219422\Omega$$

$$X_C = 30\%(0.219422\Omega) = 0.066\Omega$$

$$X_C/2 = 0.033\Omega$$

# The Capacitor as a Two-Port

---


$$V_S = V_R + (-jX_C)I_R \quad I_S = I_R$$

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} 1 & -jX_C \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & -jX_C \\ 0 & 1 \end{bmatrix} \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} 1 & -jX_C \\ 0 & 1 \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & -j0.033 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 0.8747\angle0.4412^\circ & 0.219745\angle86.99^\circ \\ 1.0704\angle90.14^\circ & 0.8747\angle0.4412^\circ \end{bmatrix} \begin{bmatrix} 1 & -j0.033 \\ 0 & 1 \end{bmatrix}$$
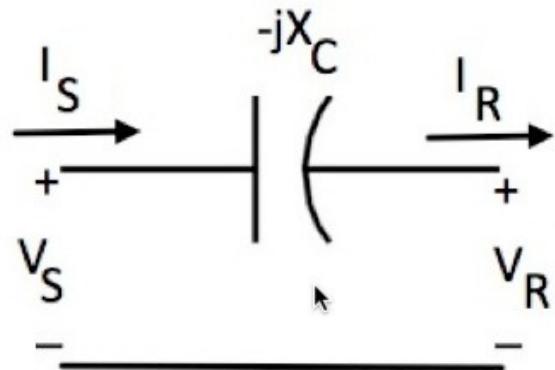
$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_{compensated} = \begin{bmatrix} 0.9100\angle0.4295^\circ & 0.1610\angle85.7385^\circ \\ 1.0704\angle90.14^\circ & 0.9100\angle0.4295^\circ \end{bmatrix}$$



# Series Compensation

---

$$1.05\angle\delta = 0.9100\angle0.4295^\circ \cdot 0.95\angle0^\circ + 0.1610\angle85.7385^\circ \cdot |I_R| \angle -36.87^\circ$$

$$1.05\angle\delta = 0.8654\angle0.4295^\circ + 0.1610 \cdot |I_R| \angle 48.8586^\circ$$

$$1.05\angle\delta - 0.4295^\circ = 0.8654\angle0^\circ + 0.1610 \cdot |I_R| \angle 48.439^\circ$$

$$1.05^2 = 0.8654^2 + (0.1610 \cdot |I_R|)^2 - 2 \cdot 0.1610 \cdot |I_R| \cdot 0.8654 \cos(131.561^\circ)$$

$$x = -8.6999 \text{ or } x = 1.56793$$

$$S_R = V_R \cdot I_R^* = (0.95\angle0^\circ \cdot 1.56793\angle -36.87^\circ)^* = 1.48953\angle36.87^\circ$$

$$P_R = p.f. |S_R| = .8 \cdot 1.48953 = 1.1916 \text{ p.u.} = 1191.6 \text{ MW}$$

Recall the uncompensated results :

$$S_R = V_R \cdot I_R^* = 0.95\angle0^\circ \cdot 1.3636\angle36.87^\circ^* = 1.29542\angle36.87^\circ$$

$$P_R = p.f. |S_R| = .8 \cdot 1.29542 = 1.0363 \text{ p.u.} = 1036.3 \text{ MW}$$

# Series Compensation - R.E. Circle Diagram

---

$$S_R = \frac{|V_R|^2 |A|}{|B|} \angle \beta - \alpha - 180 + \frac{|V_R| \cdot |V_S|}{|B|} \angle \beta - \delta$$


$$S_R = \frac{0.95^2 \cdot 0.9100}{0.1610} \angle 85.7385 - 0.4295 - 180 + \frac{0.95 \cdot 1.05}{0.1610} \angle 85.7385 - \delta$$

$$S_R = 5.1011 \angle -94.691 + 6.195652 \angle 85.7385 - \delta$$

$$6.195652^2 = 5.1011^2 + |S_R|^2 - 2 \cdot |S_R| \cdot 5.1011 \cos(131.564)$$

$$x = -8.2648 \text{ or } x = 1.4961$$
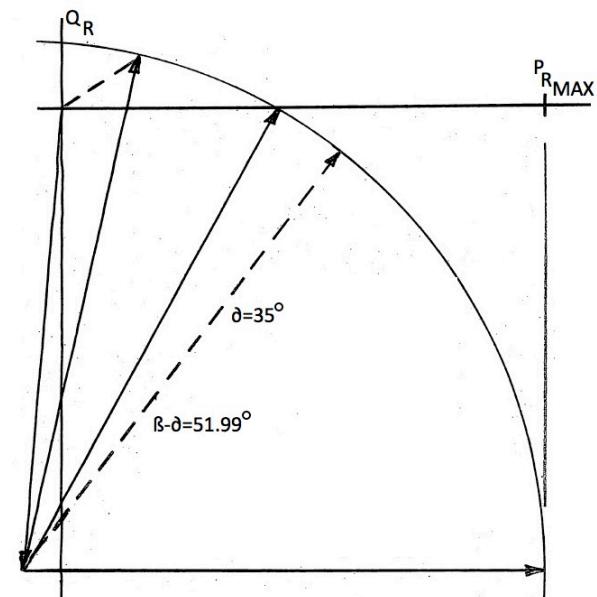
$$P_R = 0.8 \cdot S_R = 1.1969 \text{ p.u.} = 1196.9 \text{ MW}$$



# Trust No One – Test Everything!

---

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

Two test were performed on a 300km transmission line

Open Ckt Test ( $I_R=0$ )  $Z_{OC} = V_S/I_S = 991.202/-89.9722$

Short Ckt Test ( $V_R=0$ )  $Z_{SC} = V_S/I_S = 160.751/+89.4422$

$$(A \cdot D) - (B \cdot C) = 1 \quad \text{and} \quad A = D$$

$$A^2 = (B \cdot C) + 1$$

$$Z_{OC} = \frac{A}{C} = 991.202\angle -89.9722^\circ \quad \text{or} \quad C = \frac{A}{991.202\angle -89.9722^\circ}$$

$$Z_{SC} = \frac{B}{D} = \frac{B}{A} = 160.751\angle 89.4422^\circ \quad \text{or} \quad B = A \cdot 160.751\angle 89.4422^\circ$$

$$A^2 = \frac{160.751\angle 89.4422^\circ}{991.202\angle -89.9722^\circ} \cdot A^2 + 1 = 0.162178\angle 179.4144 \cdot A^2 + 1$$

$$A = 0.927609\angle 0.04086^\circ$$

$$B = 0.927609\angle 0.04086^\circ \cdot 160.751\angle 89.4422^\circ = 149.1141\angle 89.4831^\circ$$

$$C = \frac{0.927609\angle 0.04086^\circ}{991.202\angle -89.9722^\circ} = 9.3584 \cdot 10^{-4} \angle 90.0131^\circ$$

## Now Find Z (per km) and Y (per km)

---

$$A = 0.927609 \angle 0.04086^\circ$$

$$B = 149.1141 \angle 89.4831^\circ$$

$$C = 9.3584 \cdot 10^{-4} \angle 90.0131^\circ$$

$$\text{but } A = \cosh \gamma l \Rightarrow \gamma l = \cosh^{-1}(0.927609 \angle 0.04086^\circ) = 0.38284 \angle 89.7350$$

$$\gamma = \frac{\cosh^{-1}(0.927609 \angle 0.04086^\circ)}{300} = 1.2761 \cdot 10^{-3} \angle 89.7350^\circ = \sqrt{Z \cdot Y}$$

$$B = Z_C \cdot \sinh(\gamma l)$$

$$Z_C = \frac{149.1141 \angle 89.4831^\circ}{\sinh(0.38284 \angle 89.7350)} = 399.17386 \angle -0.26497 = \sqrt{\frac{Z}{Y}}$$

$$Z = Z_C \cdot \gamma = 1.2761 \cdot 10^{-3} \angle 89.7350^\circ \cdot 399.17386 \angle -0.26497 = 0.5094 \angle 89.47^\circ \Omega/km$$

$$Y = \frac{\gamma}{Z_C} = \frac{1.2761 \cdot 10^{-3} \angle 89.7350}{399.17386 \angle -0.26497} = 3.1969 \cdot 10^{-6} \angle 90^\circ S/km$$