

Name KEY

E-mail \_\_\_\_\_

$\frac{1}{2} \cdot \frac{1}{2} = \frac{1}{4}$   
 $\frac{1}{2} \cdot \frac{1}{2} = \frac{1}{4}$   
 $\frac{1}{2} \cdot \frac{1}{2} = \frac{1}{4}$

EE 4221

Hour Exam 1

October 5, 2017

Directions:

1. DO NOT START until told to do so.
2. There are 4 problems in this examination. All problems are equal valued.
3. The correct answer is a necessary but not sufficient condition to receive full credit for a problem. You MUST show you work! Disorderly or illegible work cannot and thus will not be graded.
4. The exam is "closed notes/closed book". You are however allowed use of an 8.5" x 11.0" formula sheet of your own design as a reference during the exam.
5. The exam duration is 70 (seventy) minutes.

1. A single phase load is supplied by a sinusoidal voltage  $v(t) = 200\cos(377t)V$ .  
The resulting instantaneous power is  $p(t) = 800 + 1000 \cos(754t - 36.87^\circ)W$ . Determine:

a) The average real power consumed by the load.

$$P = 800W$$

b) The reactive power associated with the load.

$$Q = -600VAR$$

c) A time domain expression for the current flowing through the load

$$I = \left( \frac{S}{V_{RMS}} \right)^* \left( \frac{1000 \angle -36.87}{\frac{200 \angle 0^\circ}{\sqrt{2}}} \right)^* = \sqrt{2} 5 \angle 36.87 \text{ A}_{RMS}$$


$$10 \cos(754t + 36.87^\circ) \text{ A}$$

d) The value of the load impedance

$$\frac{200 \angle 0^\circ}{10 \angle 36.87} = 20 \angle -36.87^\circ = 16 - j12 \Omega$$

$$\begin{aligned} \text{do } |I_{RMS}|^2 \cdot R &= P & (\sqrt{2} 5)^2 \cdot 16 &= 800W & \text{YES!} \\ |I_{RMS}|^2 \cdot X_L &= Q & (\sqrt{2} 5)^2 \cdot -12 &= -600VAR & \end{aligned}$$

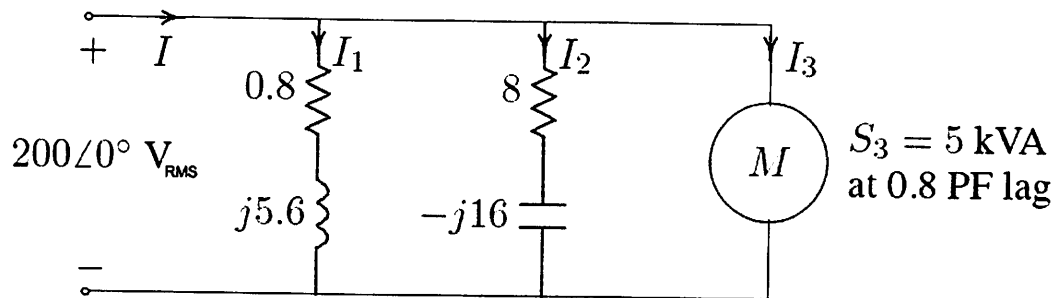2. Two impedances,  $Z_1 = 0.8 + j5.6\Omega$  and  $Z_2 = 8.0 - j16.0\Omega$  and a single phase motor are connected in parallel with a 200VRMS, 60 Hz supply as shown below. The motor draws 5kVA at a p.f. of 0.8 lagging. Determine:



a) The composite power triangle that represents the total combined load.


$$I_1 = \frac{200}{0.8 + j5.6} = 35.36 \angle -81.87^\circ$$

$$S_1 = 200 \times 35.36 \angle +81.87^\circ = 7071.07 \angle 81.87^\circ$$

$$I_2 = \frac{200}{8 - j16} = 11.18 \angle 63.43^\circ$$

$$S_2 = 200 \times 11.18 \angle -63.43^\circ = 2236.07 \angle -63.43^\circ$$
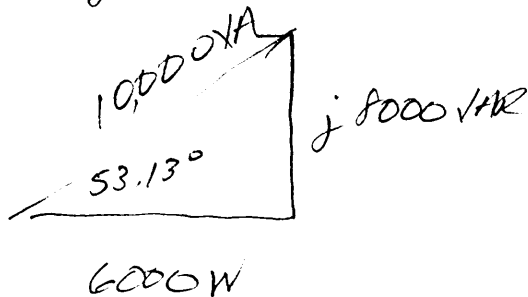
$$S_3 = 5000 \angle 37.87^\circ = 4000 + j3000$$





b) the value of a single paralleled capacitor (in Farads) that when added to the system would improve the overall power factor to unity.

$$Q_{cap} = -8000 \text{ VAR for unity pf} = \frac{V_{RMS}^2}{X_C}$$

$$X_C = \frac{200^2}{8000} = 5 = \frac{1}{\omega C} \Rightarrow C = \frac{1}{2\pi(60) \times 5} = 530.5 \mu\text{F}$$

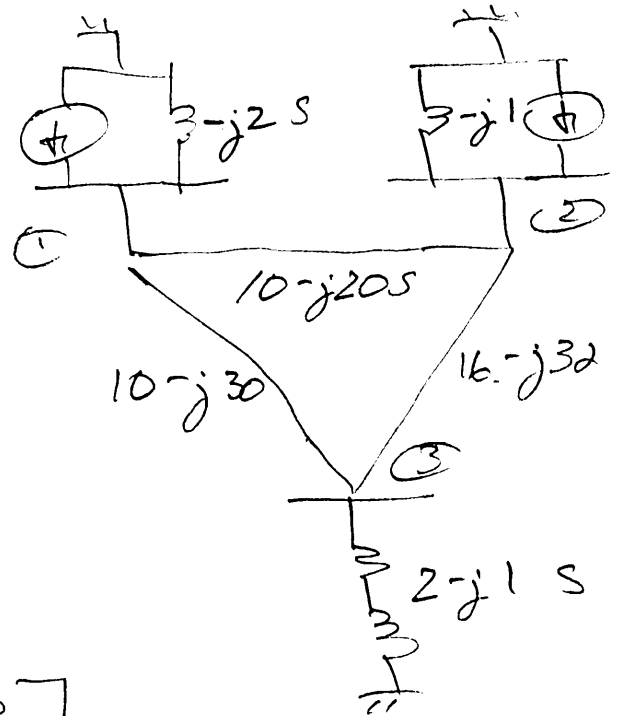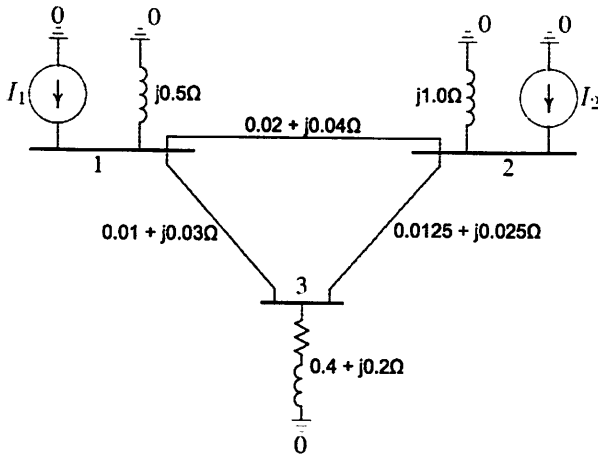
3. The **impedance diagram** for a three bus power system is shown below. The impedance of the transmission lines that interconnect the busses is also noted.

Construct the **admittance diagram** for the circuit and determine the Ybus matrix that could be used to solve for the bus voltages in the system.




$$\begin{bmatrix} 20-j52 & -10+j20 & -10+j30 \\ -10+j20 & 26-j53 & -16+j32 \\ -10+j30 & -16+j32 & 28-j63 \end{bmatrix} = Y_{Bus}$$

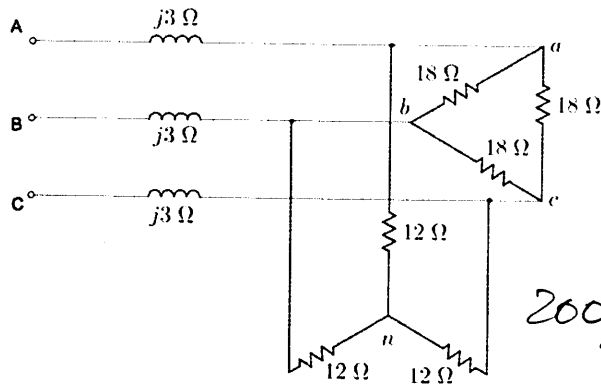4. An A-B-C positive phase sequence 60Hz three phase generator feeds a paralleled wye / delta load through a transmission line with impedance ( $z_{line} = j3.0 \Omega$ ). Given the voltage between the A and B lines at the generator,  $V_{AB} = 346.41/\underline{30^\circ}$  V RMS determine:


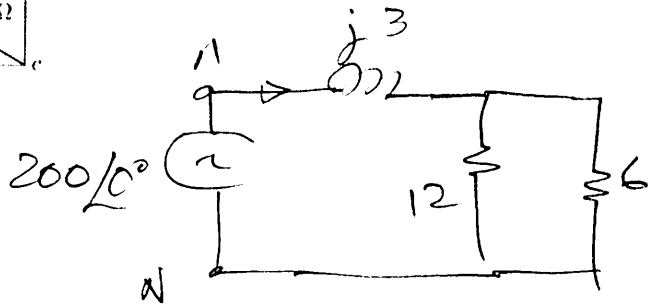
$$Z_{eq} = \frac{Z_{\Delta}}{3} = 6 \Omega$$



a). The total apparent power supplied by the three phase source.

$$\bar{I}_S = \frac{200 \angle 0^\circ}{4 + j3} = 40 \angle -36.87^\circ$$

$$S_{\phi} = \bar{V}_{AN} \bar{I}_S^* = 200 \angle 0^\circ \times 40 \angle 36.87^\circ = 8000 \angle 36.87^\circ$$

$$S_T = 3S_{\phi} = 24,000 \angle 36.87^\circ \text{ VA}$$

b). The load side line voltage  $V_{ab}$

$$\begin{aligned} \bar{V}_{an} &= \bar{V}_{AN} - j3 \bar{I}_S = 200 \angle 0^\circ - (j3)(40 \angle -36.87^\circ) \\ &= 160 \angle -36.87^\circ \end{aligned}$$

$$V_{ab} = \sqrt{3} 160 \angle -36.87^\circ + 30^\circ = 277.13 \angle -6.87^\circ$$